

Oscillators

An oscillator is a circuit which produces a continuous, repeated, alternating wave-form (a.c) without any input.

Oscillators basically convert unidirectional current flow from a d.c. source into an alternating waveform which is of the desired frequency, as decided by its circuit components.

Positive feedback.

Fig. shows the block diagram of an amplifier with positive feedback applied.

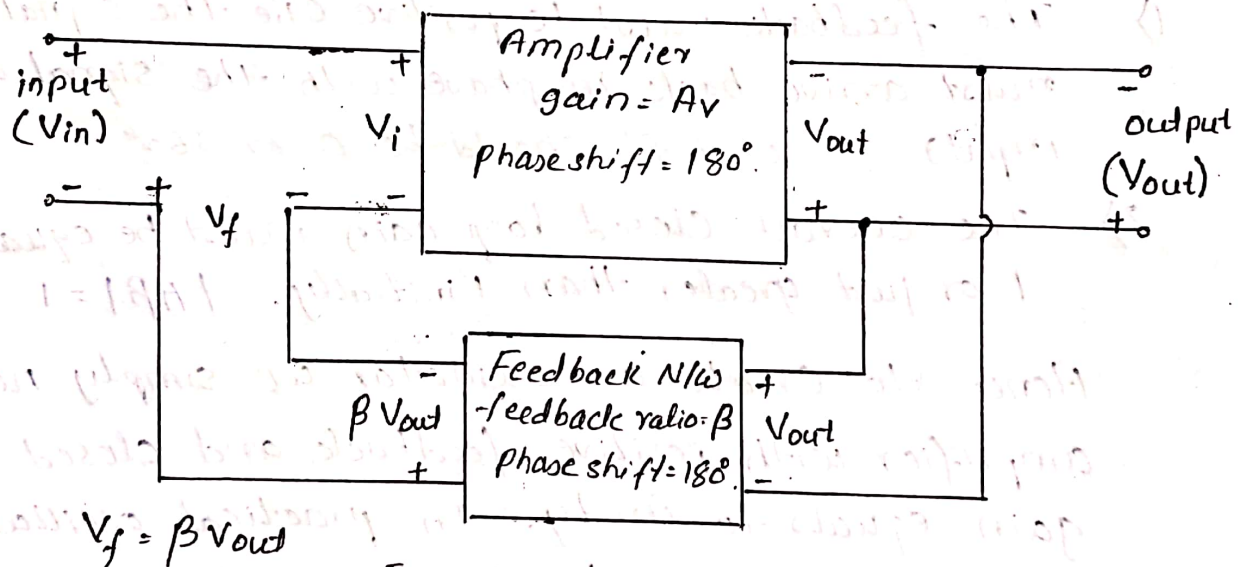


Fig. Amplifier with positive feedback.

Note that the amplifier provides a phase shift of 180° and the feedback network provides a further phase shift of 180° . Thus, the overall phase shift is 360° or 0° .

The overall voltage gain, G is given by

$$G = \frac{V_{out}}{V_{in}}$$

By KVL at input.

$$V_i = V_{in} + \beta V_{out}$$

Thus, $V_{in} = V_i - \beta V_{out}$ and

$$V_{out} = A_v \times V_{in}$$

$$\therefore A_v = \frac{V_{out}}{V_i}$$

$$\therefore G = \frac{A_v \times V_i}{V_i - \beta V_{out}} = \frac{A_v}{V_i - \beta A_v \times V_i}$$

$$\text{Thus } \boxed{G = \frac{A_v}{1 - \beta A_v}}$$

This shows that with positive feedback overall gain G of the amplifier increases.


* Conditions for Oscillations. (Barkhausen Criterion)
Conditions for oscillations are.

- 1) The feedback must be positive (i.e. the signal feedback must arrive back in-phase with the signal at the input). phase shift should be 0° or 360°
- 2) The overall closed loop gain must be equal to 1 or just greater than 1 initially. $|A\beta| = 1$

Hence to create an oscillator we simply need an amplifier with positive feedback and closed loop gain equals to unity. In practical oscillator, it is not necessary to supply an input signal to start oscillation, instead oscillations are self starting and begin oscillations as soon as dc power is applied.

Ladder network oscillator.

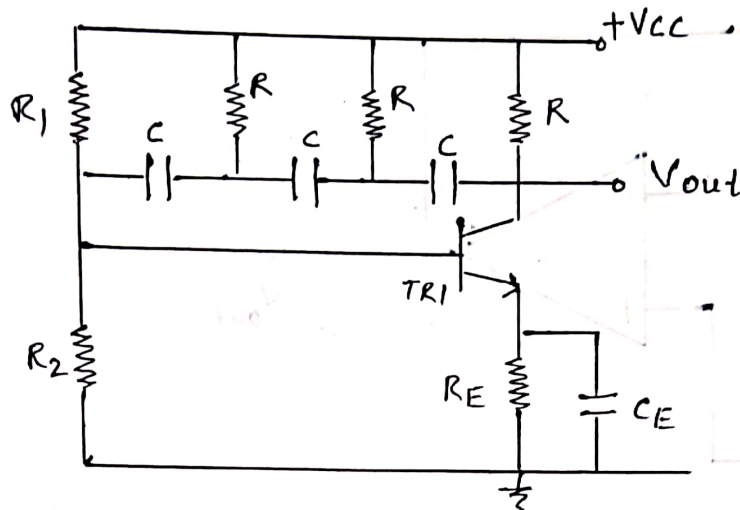A simple phase-shift oscillator based on a three-stage R-C ladder network is shown in fig.



TR₁ operates as common-emitter amplifier stage with R₁ and R₂ providing base bias and R_E and C_E providing emitter stabilization.

The total phase shift provided by the R-C ladder network is 180° at the frequency of oscillation. The transistor provides the other 180° phase shift in order to realize an overall phase shift of 360° or 0°.

The frequency of oscillation of the circuit shown in fig. is given by

$$f = \frac{1}{2\pi\sqrt{6}RC} \text{ Hz.}$$

The loss associated with ladder network is 29.

Thus the amplifier must provide at least gain of 29 in order for the ckt to oscillate.


Ex: determine the frequency of oscillation of a three-stage ladder network oscillator in which C = 10 nF & R = 10 kΩ.

Soln: w.k.T.


$$f = \frac{1}{2\pi\sqrt{6}RC} = \frac{1}{6.28 \times 2.45 \times 10 \times 10^3 \times 10 \times 10^{-9}}$$
$$= 647 \text{ Hz.}$$

Wien Bridge Oscillator.

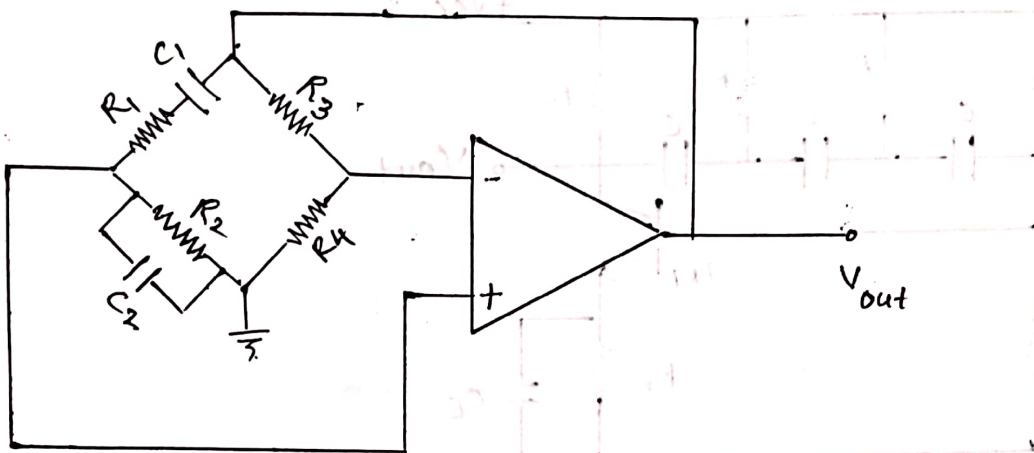The wien bridge oscillator is shown in fig. below.



OR

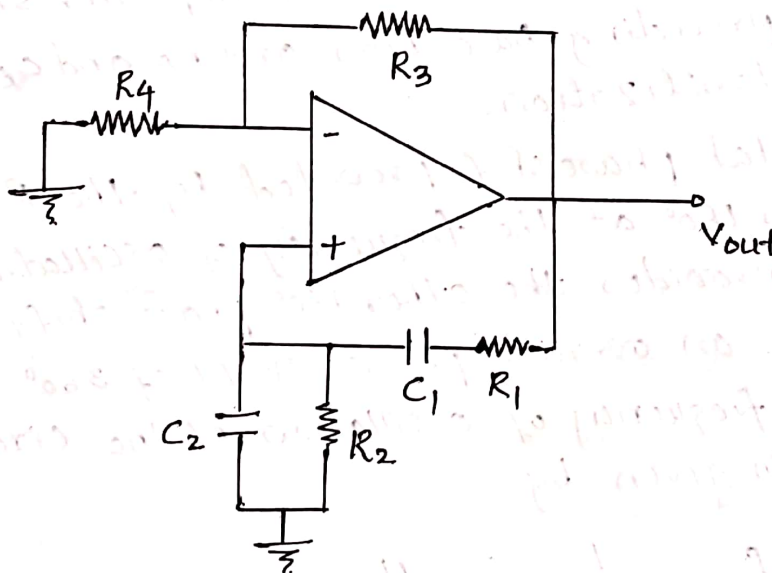

The feedback network comprises of a wien bridge circuit. The opamp is used in non inverting configuration. Oscillation occurs at the frequency for which the phase shift through wien bridge is 0° , because amplifier is in non inverting mode.

When $R_1 = R_2$ and $C_1 = C_2$, the frequency of oscillation is given by.

$$f = \frac{1}{2\pi RC} \text{ Hz.}$$

Ex: In Wien bridge oscillator if $C_1 = C_2 = 100\text{ nF}$, determine the output frequencies when i) $R_1 = R_2 = 1\text{ k}\Omega$ & ii) $R_1 = R_2 = 6\text{ k}\Omega$.

Soln: i) When $R_1 = R_2 = 1\text{ k}\Omega$.

$$f = \frac{1}{2\pi RC} \quad \text{where } R = R_1 = R_2 \text{ and } C = C_1 = C_2$$

$$\therefore f = \frac{1}{2\pi \times 1 \times 10^3 \times 100 \times 10^{-9}} = 1.59\text{ kHz.}$$

ii) When $R_1 = R_2 = 6\text{ k}\Omega$.

$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 6 \times 10^3 \times 100 \times 10^{-9}} = 265\text{ Hz.}$$

* Multivibrator


An electronic circuit that produces a non-sinusoidal waveform as its output is known as a multivibrator. The waveform are basically a square wave, rectangular wave etc.

The basic types of multivibrator are:

- Astable multivibrator that provides a continuous train of pulses. These are also referred to as free-running multivibrators.
- Monostable multivibrators that produce a single output pulse. They have one stable state and thus sometimes also referred to as ~~one-state~~ 'one-shot'.
- Bistable multivibrators that have two stable states and require a trigger pulse or control signal to change from one state to other.

* Single-stage astable Oscillator

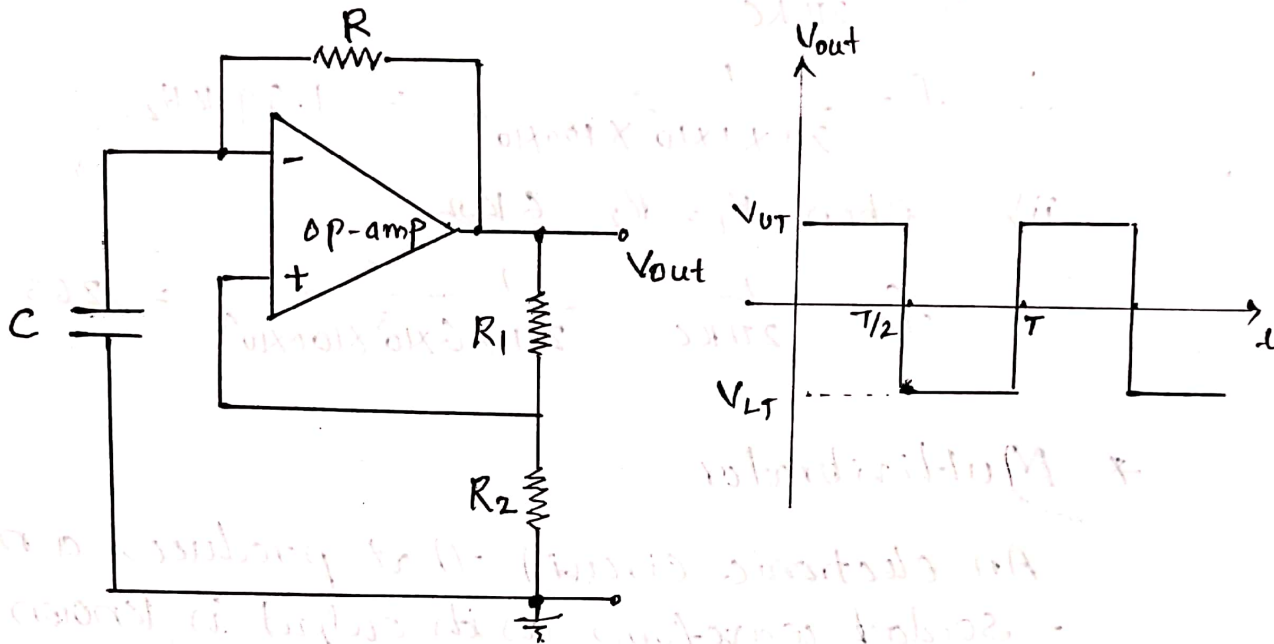A simple form of astable oscillator that produces a square wave output can be built using just one op-amp, as shown in fig.



The circuit employs positive feedback with output fed back to the non-inverting input via the voltage divider formed by R_1 and R_2 .

The upper threshold voltage will be given by

$$V_{UT} = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

The lower threshold voltage will be given by

$$V_{LT} = -V_{CC} \times \frac{R_2}{R_1 + R_2}$$

Finally, the time for one complete cycle of the output waveform produced by the astable oscillator is given by.


$$T = 2RC \ln \left(1 + 2 \left(\frac{R_2}{R_1} \right) \right)$$

$$\text{Frequency, } F = \frac{1}{T}$$


* Crystal Controlled Oscillator.

A crystal oscillator is an electronic oscillator circuit that uses piezoelectric effect of crystal material to create an electrical signal with constant frequency.

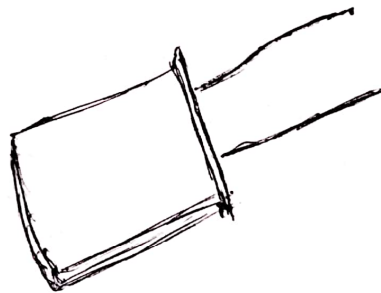A quartz crystal can be used as the frequency determining element. The quartz crystal (a thin slice of quartz in hermetically sealed enclosure) is shown in fig. vibrates whenever a potential



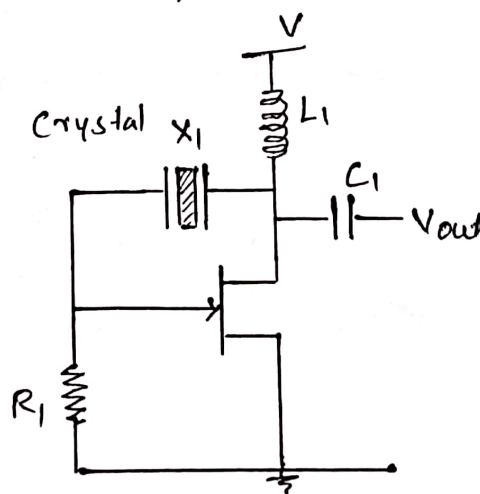difference is applied across its faces. This phenomenon is known as the piezoelectric effect. The frequency of oscillation is determined by the crystal's 'cut' and physical size. Crystal oscillator provides stabilized frequency of oscillations. Fig shown below is a simple crystal oscillator circuit.



prof. RAMESH PATIL
E&CE dept
GNDEC, Bidar.