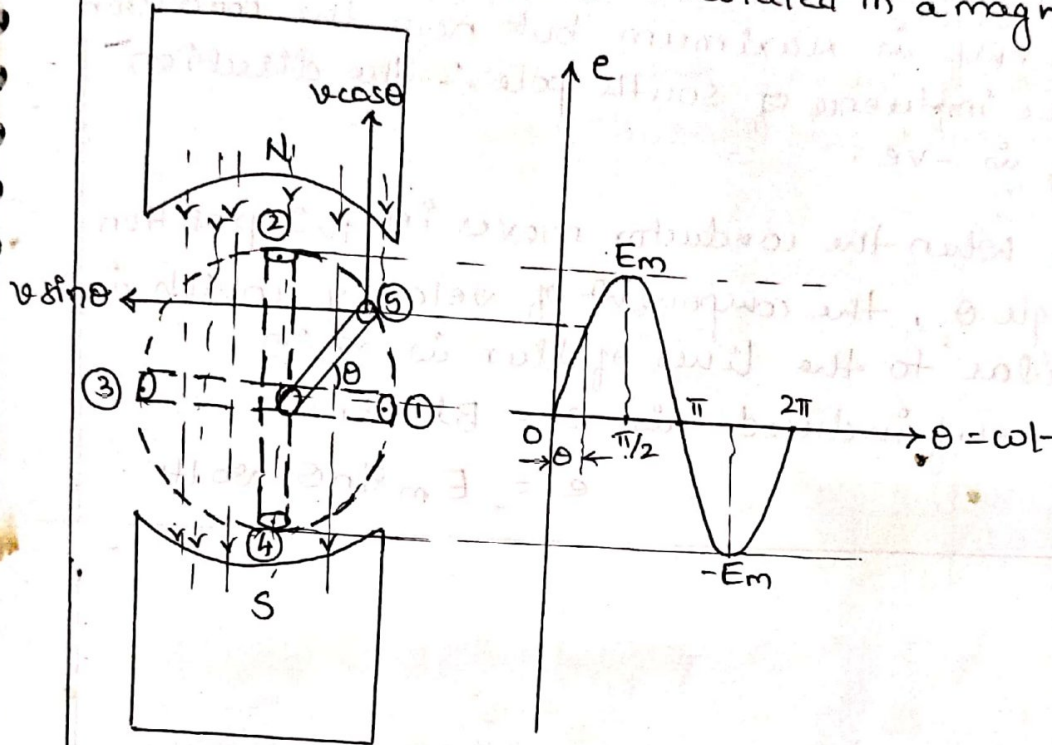


Module I

2) A.C. FUNDAMENTALS

Generation of sinusoidal voltage :-

Q1) With a neat sketch explain how an alternating voltage is produced when a coil is rotated in a magnetic field. (6m)



Position 1 :- consider a magnetic field of constant flux density B wb/m^2 .

Let a conductor of length l is placed in a magnetic field with velocity v m/s .

Position 1 :- At this position the motion of the conductor is parallel to the lines of flux. Hence flux cut by the conductor is zero & induced emf is also zero.

Position 2 :- At this position the motion of the conductor is perpendicular to the lines of flux. Hence flux cut by the conductor is maximum & the induced emf is also maximum.

Position 3 :- At this position again the motion of the conductor is parallel to the lines of flux hence the induced emf is zero.

Position 4 :- At this position the motion of the conductor is perpendicular to the lines of flux & the induced emf is maximum but now the conductor is under the influence of south pole $\therefore$ the direction of the emf is -ve.

Position 5 :- When the conductor moves in this position making angle θ , the component of velocity which is perpendicular to the lines of flux is $v \sin \theta$.

Hence the emf induced is $e = Blv \sin \theta$.

$$e = E_m \sin \theta \text{ volt.}$$

Module II

i) Single Phase AC Circuits

Definitions :-

i) RMS Value $\Rightarrow$

The RMS value of an AC is equal to that DC which produces same amount of heat as produced by AC when passed through the same resistance for the same time.

$$I = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

ii) Average value of an AC:-

The average value of an AC is equal to that DC which transfers same amount of charge as by AC for the same circuit in same time.

$$I_{avg} = \frac{2I_m}{\pi} = 0.637 I_m$$

iii) Form factor:-

It is the ratio of RMS value to the average value of an A.C quantity.

$$\text{ie; form factor} = \frac{\text{RMS value}}{\text{Avg value}} = \frac{0.707 I_m}{0.637 I_m}$$

$$k_f = 1.11$$

iv) Peak factor:-

It is the ratio of Maximum value to the RMS value of an A.C quantity.

$$\text{ie; peak factor} = \frac{\text{Max. value}}{\text{RMS value}} = \frac{I_m}{0.707 I_m}$$

$$k_p = 1.414$$

Frequency of Generated voltage :-


Define the following :-
i) frequency ii) Time period
iii) Instantaneous value iv) Amplitude.

i) Frequency (f) :-

It is defined as
Number of cycles completed
by an a.c per second:

$$\text{ie; } f = \frac{1}{T} \text{ Hz}$$

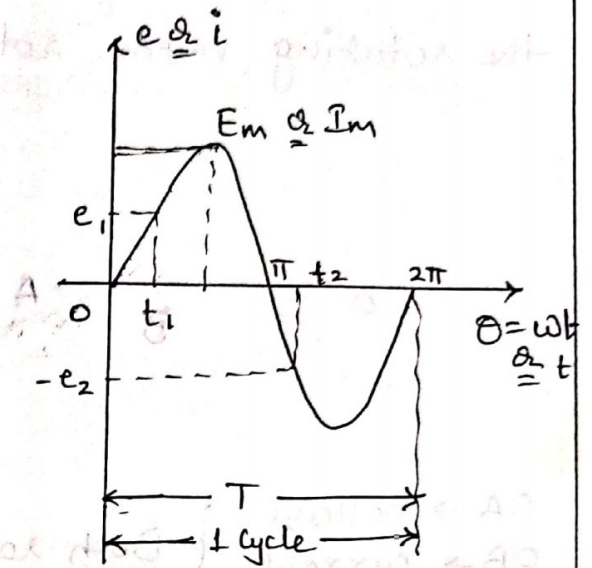It is represented as f and
its unit is Hz.



ii) Time Period (T) :-

It is defined as the time taken by an a.c
to complete its one cycle.

$$T = \frac{1}{f} \text{ sec.}$$

iii) Instantaneous value :- It is defined as

the value of an a.c at a particular instant.

Ex :- e_1 & $-e_2$ at t_1 & t_2 .


iv) Amplitude :- The Maximum value of any alternating
quantity is known as Amplitude.

Ex :- E_m & I_m .

Phase representation of an alternating quantity

Defⁿ:

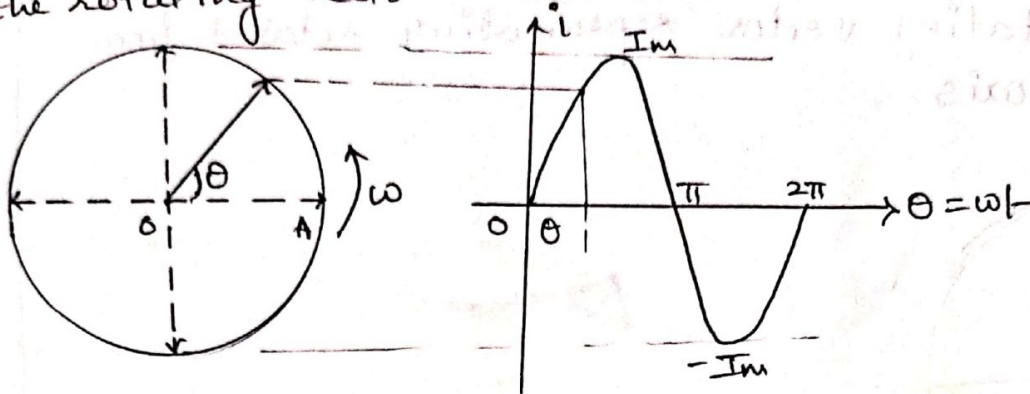
The phase of an ac is the angle through which the rotating vector rotated from the reference axis.



Phase difference:

Defⁿ:

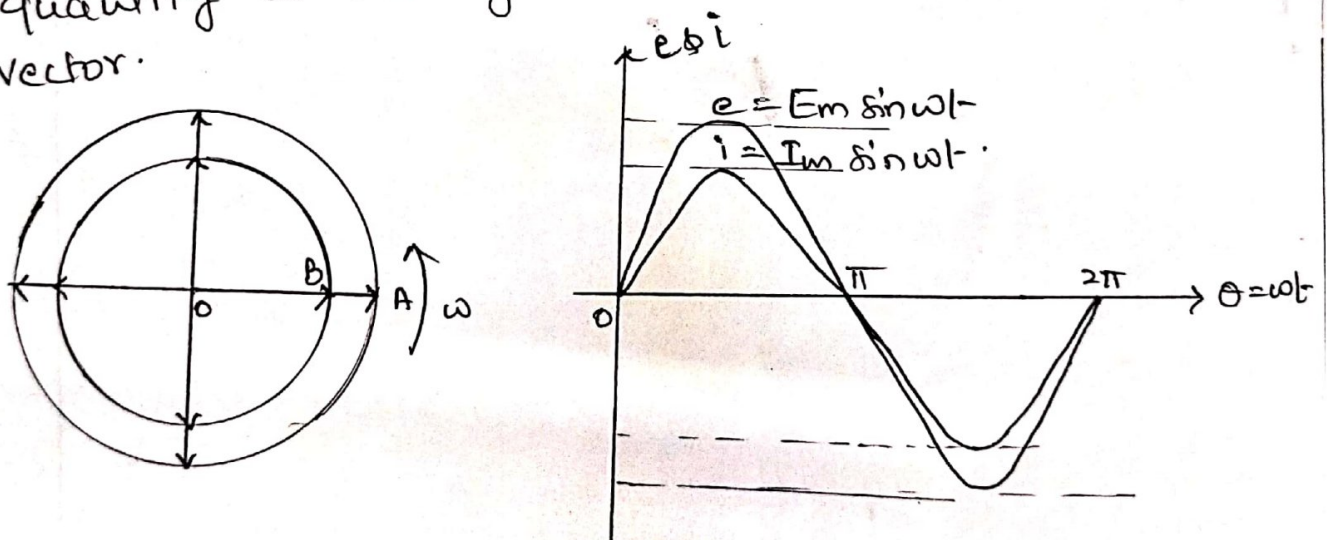The phase difference betⁿ two alternating quantity is the angle difference betⁿ the two rotating vector.




OA $\rightarrow$ voltage
OB $\rightarrow$ current

} Both rotate together with an angular velocity ω .

$\therefore$ The phase difference betⁿ them is zero.

ie; $e = E_m \sin \omega t$ Φ


$i = I_m \sin \omega t$

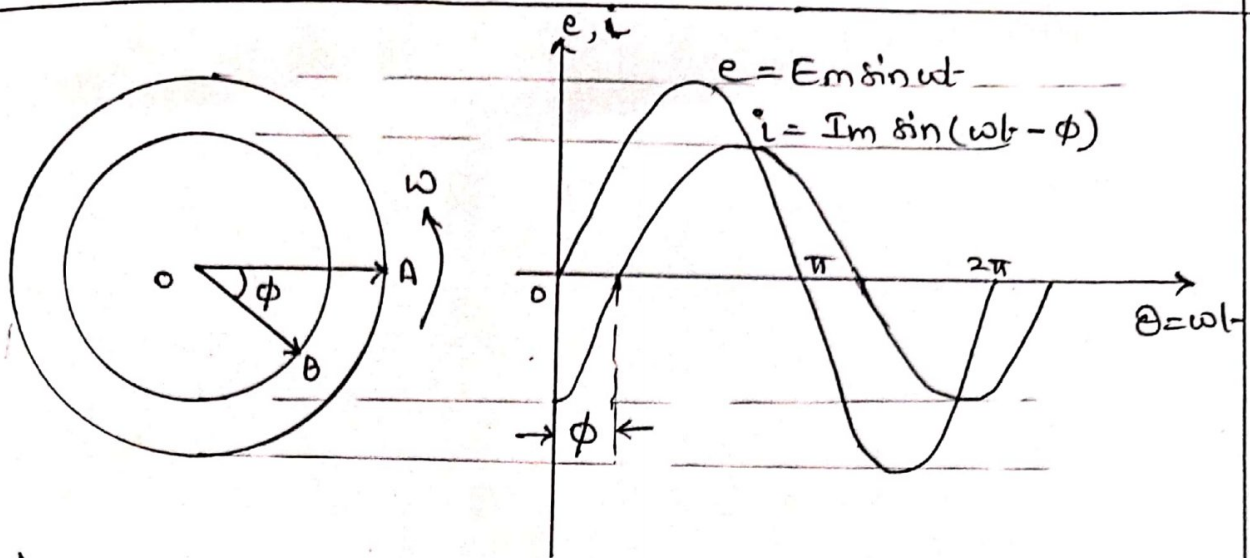

$\vec{OA} \rightarrow$ voltage
 $\vec{OB} \rightarrow$ current } Current is lagging the voltage by an angle ϕ .

$$\therefore e = E_m \sin \omega t$$

$$\& i = I_m \sin(\omega t - \phi)$$

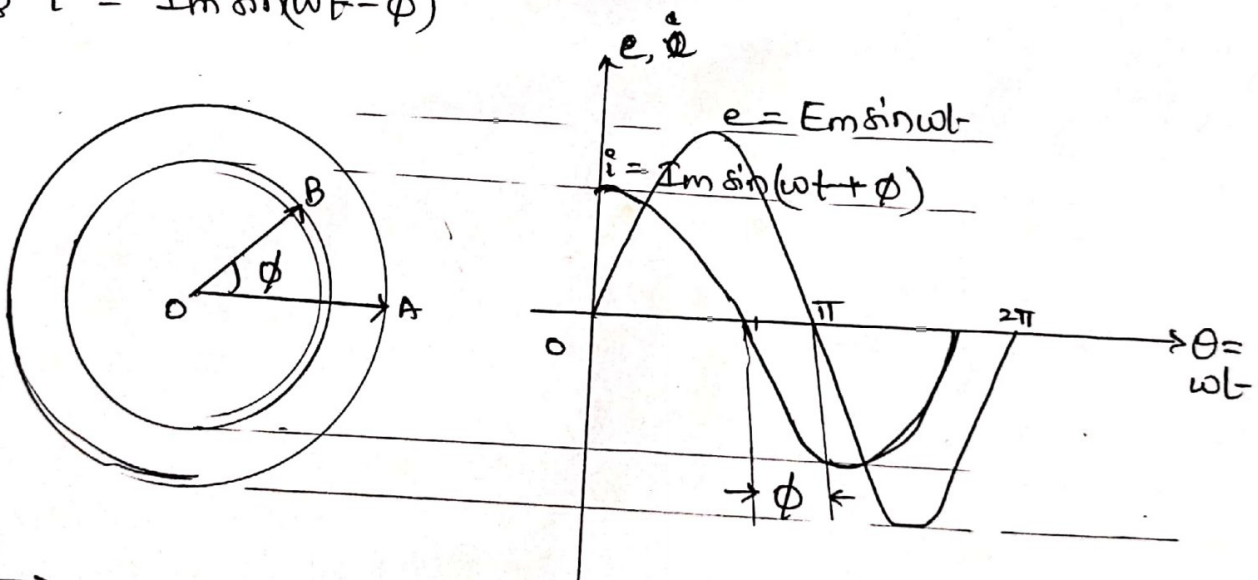

$\vec{OA} \rightarrow$ voltage
 $\vec{OB} \rightarrow$ current } Current is leading the voltage by an angle ϕ

$$\therefore e = E_m \sin \omega t$$

$$\& i = I_m \sin(\omega t + \phi)$$

1) Analysis with phasor diagram of
 1) Resistance circuit (R-circuit).

Q1) With the help of phasor diagram and waveform comment on the phase relation between voltage and current in purely resistive circuit.


OR

Derive an expression for the instantaneous power in a pure resistor energised by sinusoidal voltage.

$$e = E_m \sin \omega t \quad \text{--- (1)}$$

By Ohm's Law.

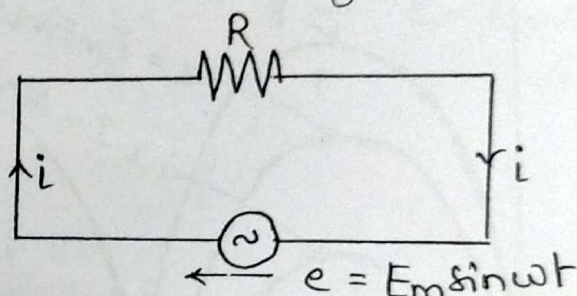
$$i = \frac{e}{R} = \frac{E_m \sin \omega t}{R}$$



$$i = I_m \sin \omega t \quad \text{--- (2)} \quad [\because I_m = E_m/R]$$

from eqⁿ. (1) & (2)
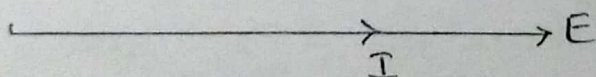
$$\left. \begin{array}{l} e = E_m \sin \omega t \\ i = I_m \sin \omega t \end{array} \right\} \text{ Hence the current and voltage are in phase in a purely resistive circuit.}$$



WKT :- $P = e i = E_m \sin \omega t \cdot I_m \sin \omega t = E_m I_m \sin^2 \omega t$

$$P = E_m I_m \left[\frac{1 - \cos 2\omega t}{2} \right]$$

$$P = \frac{1}{2} E_m I_m - \frac{1}{2} E_m I_m \cos 2\omega t \quad \text{--- (3)}$$

In above eqⁿ. the second part is


- *> Periodically varying quantity
- *> Its frequency is twice the applied voltage frequency.
- *> Its average voltage over a period of time is zero.

$$\therefore P = \frac{1}{2} E_m I_m$$

$$= \frac{E_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$

$$\boxed{P = EI} \text{ watts.}$$
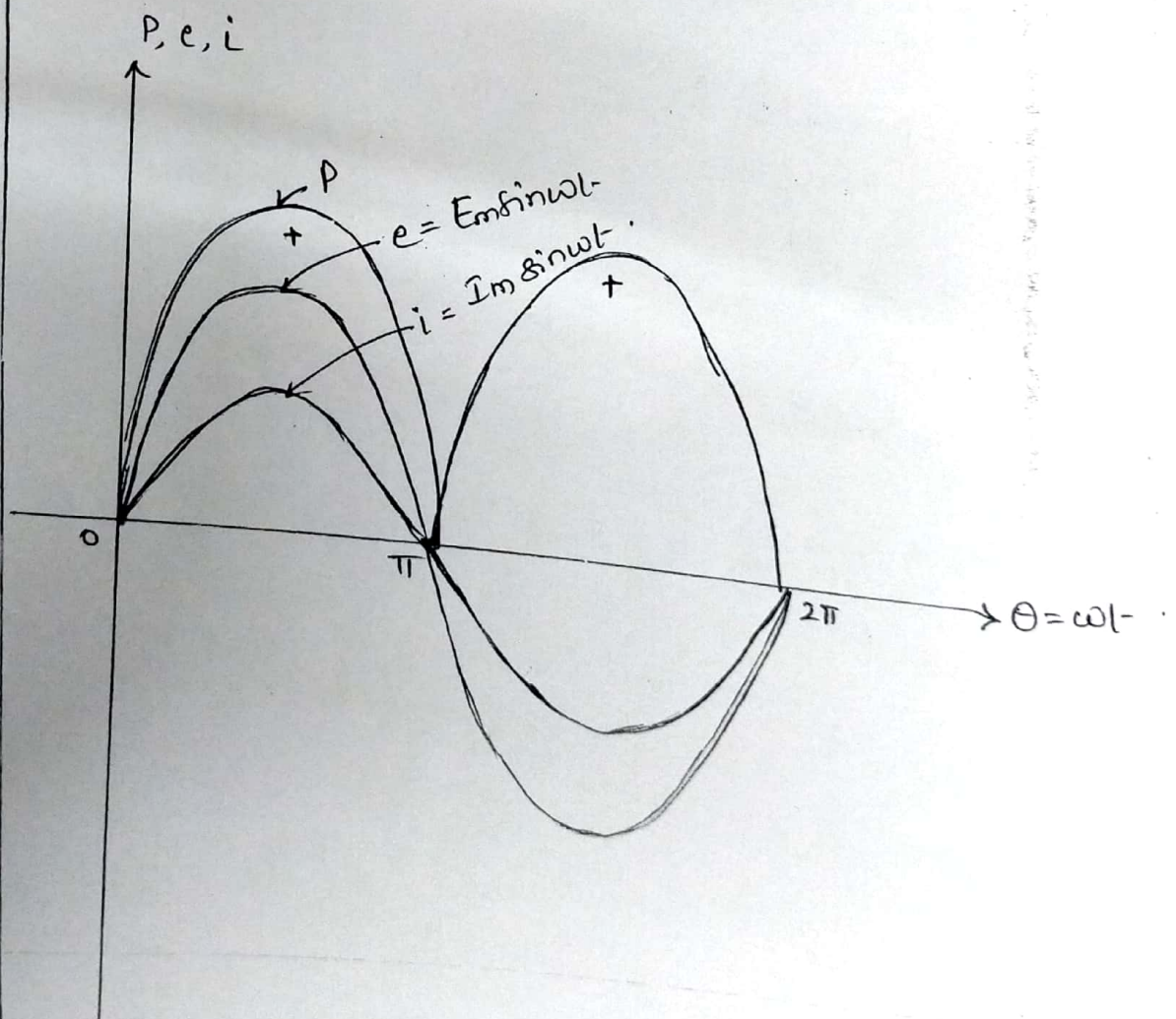
$$\left\{ \begin{array}{l} \therefore \frac{E_m}{\sqrt{2}} = E_{rms} = E \\ \& \frac{I_m}{\sqrt{2}} = I_{rms} = I \end{array} \right\}$$



2) Pure Inductive circuit :- (1-circuit)

Q2) Prove that in a purely inductive circuit current lags voltage by 90° .

Q
Prove that in a purely inductive circuit power consumed by the circuit is zero.

Wkt :- $e = E_m \sin \omega t$ — (1)

From Faraday's law

$$e' = -L \frac{di}{dt} = -e$$

$$\therefore e = L \frac{di}{dt}$$

$$di = \frac{e}{L} dt = \frac{E_m}{L} \sin \omega t dt$$

$$i = \frac{E_m}{L} \int \sin \omega t dt = \frac{E_m}{\omega L} (-\cos \omega t)$$


$$i = \frac{E_m}{\omega L} \sin(\omega t - \pi/2) = \frac{E_m}{X_L} \sin(\omega t - \pi/2)$$

$$i = I_m \sin(\omega t - \pi/2) \text{ — (2) } \left(\because I_m = \frac{E_m}{X_L} \right)$$

where $X_L = \omega L = 2\pi f L$

$X_L \rightarrow$ Inductive reactance in Ω .


From eqⁿ (1) & (2)

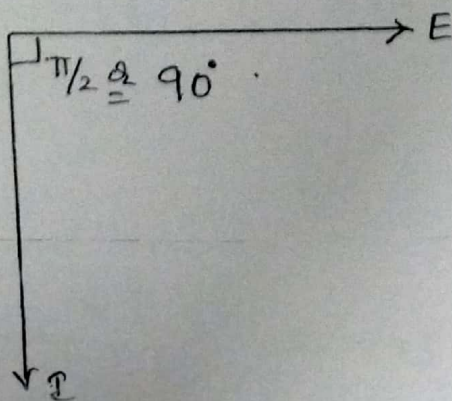

$$e = E_m \sin \omega t$$

$$i = I_m \sin(\omega t - \pi/2)$$

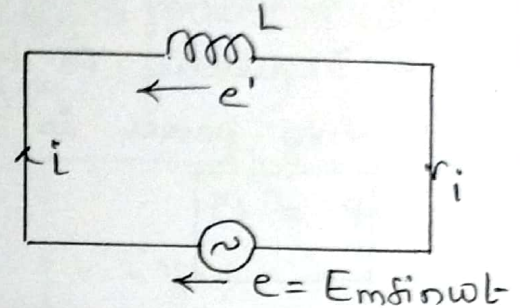Comment :- current lags voltage by an angle $90^\circ \text{ or } \pi/2$



Wkt: $P = e i = E_m \sin \omega t - I_m \sin(\omega t - \pi/2)$

$$P = E_m I_m \sin \omega t (-\cos \omega t)$$


$$P = -\frac{1}{2} E_m I_m \sin 2\omega t \quad \text{--- (3)}$$

$$\left\{ \begin{array}{l} \text{ie; } \sin A \cos B = \\ \frac{1}{2} [\sin(A+B) + \sin(A-B)] \end{array} \right\}$$

The eqⁿ (3) is

- *> Periodically varying quantity.
- *> Frequency is twice the supply frequency
- *> Avg power is zero over a period.

$$\therefore \boxed{P = 0} //$$

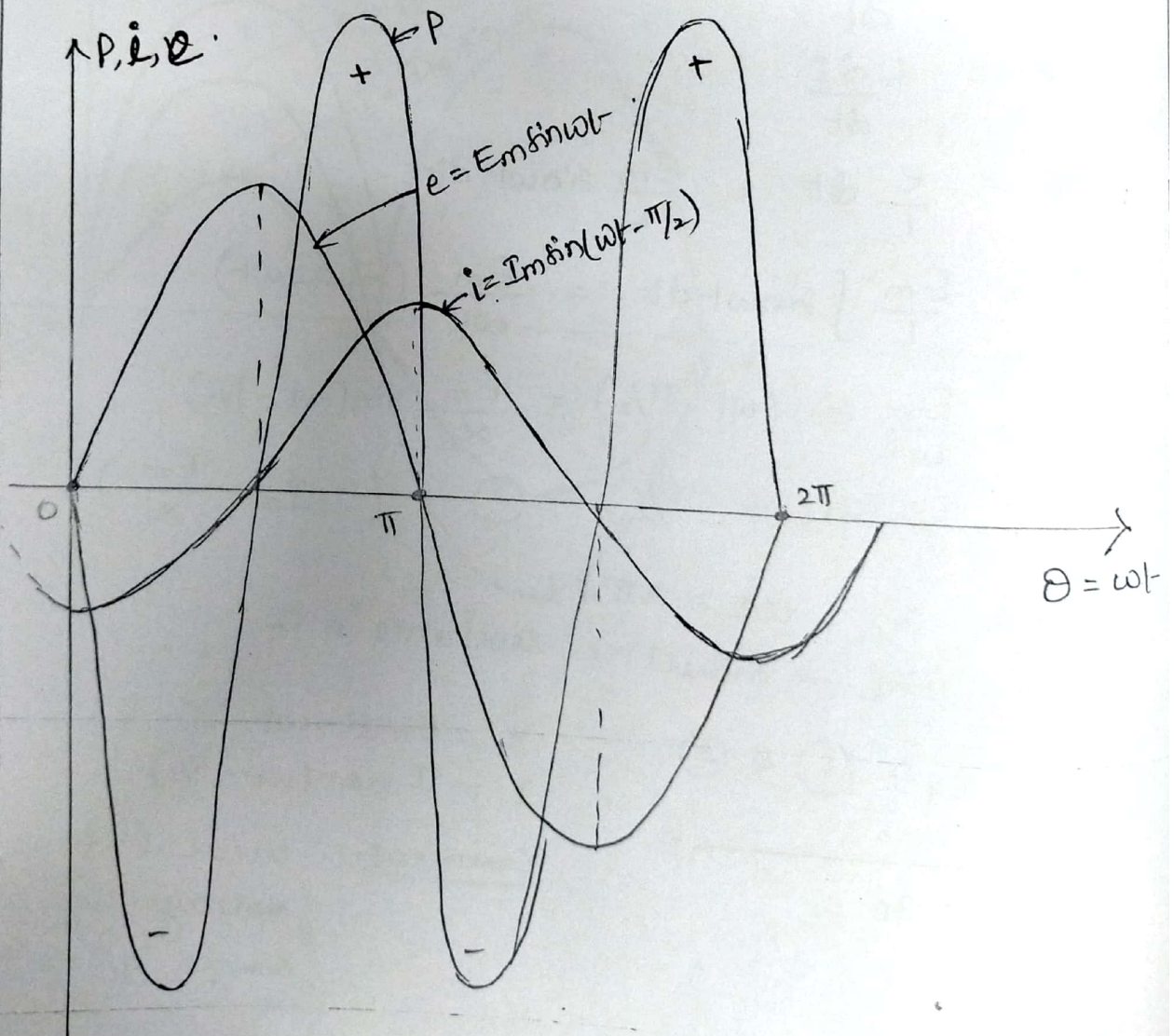

3) Pure Capacitive circuit (c-ckt) :-

Q3) With the help of neat waveform and phasor diagram show that in a pure capacitance the current leads the voltage by 90° .

or

Show that the power consumed by a pure capacitance is zero with neat circuit diagram.

wkt :- $e = E_m \sin \omega t$ — (1)

wkt :- $i = \frac{dq}{dt} = \frac{d[ce]}{dt}$

$$i = c \frac{de}{dt} = \frac{c d E_m \sin \omega t}{dt}$$

$$i = c \omega E_m \cos \omega t$$

$$= \omega c E_m (\sin(\omega t + \pi/2))$$



$$= \frac{E_m}{\frac{1}{\omega c}} \sin(\omega t + \pi/2) = \frac{E_m}{X_c} \sin(\omega t + \pi/2)$$

$$i = I_m \sin(\omega t + \pi/2) \text{ — (2) } \left[\because I_m = \frac{E_m}{X_c} \right]$$

where $X_c = \frac{1}{\omega c} = \frac{1}{2\pi f c}$

$X_c \rightarrow$ capacitive reactance in Ω .

from eqⁿ (1) & (2)

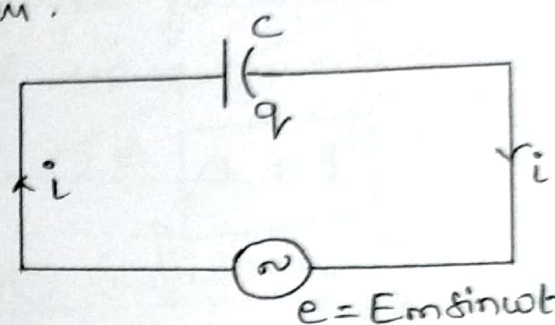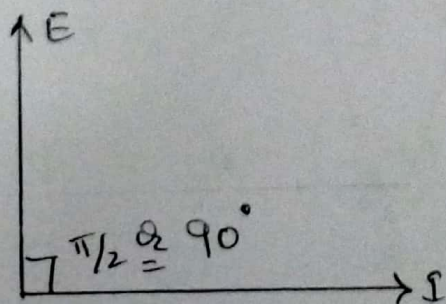

$$\left\{ \begin{array}{l} \because q = ce \\ \therefore c = q/e \\ \text{or } e = q/c \end{array} \right.$$

Wkt :- $P = ei = E_m \sin \omega t - I_m \sin(\omega t + \pi/2)$

$$P = E_m I_m \sin \omega t \cos \omega t$$


$$P = \frac{1}{2} E_m I_m \sin 2\omega t \quad \text{--- (3)}$$

$$\left\{ \begin{array}{l} \because \sin A \cos B = \\ \sin(A+B) + \sin(A-B) \end{array} \right.$$

The eqⁿ (3) is

- *> Periodically varying quantity
- *> Frequency is twice the supply frequency.
- *> average power is zero over a period.

$\therefore \boxed{P = 0}$ //

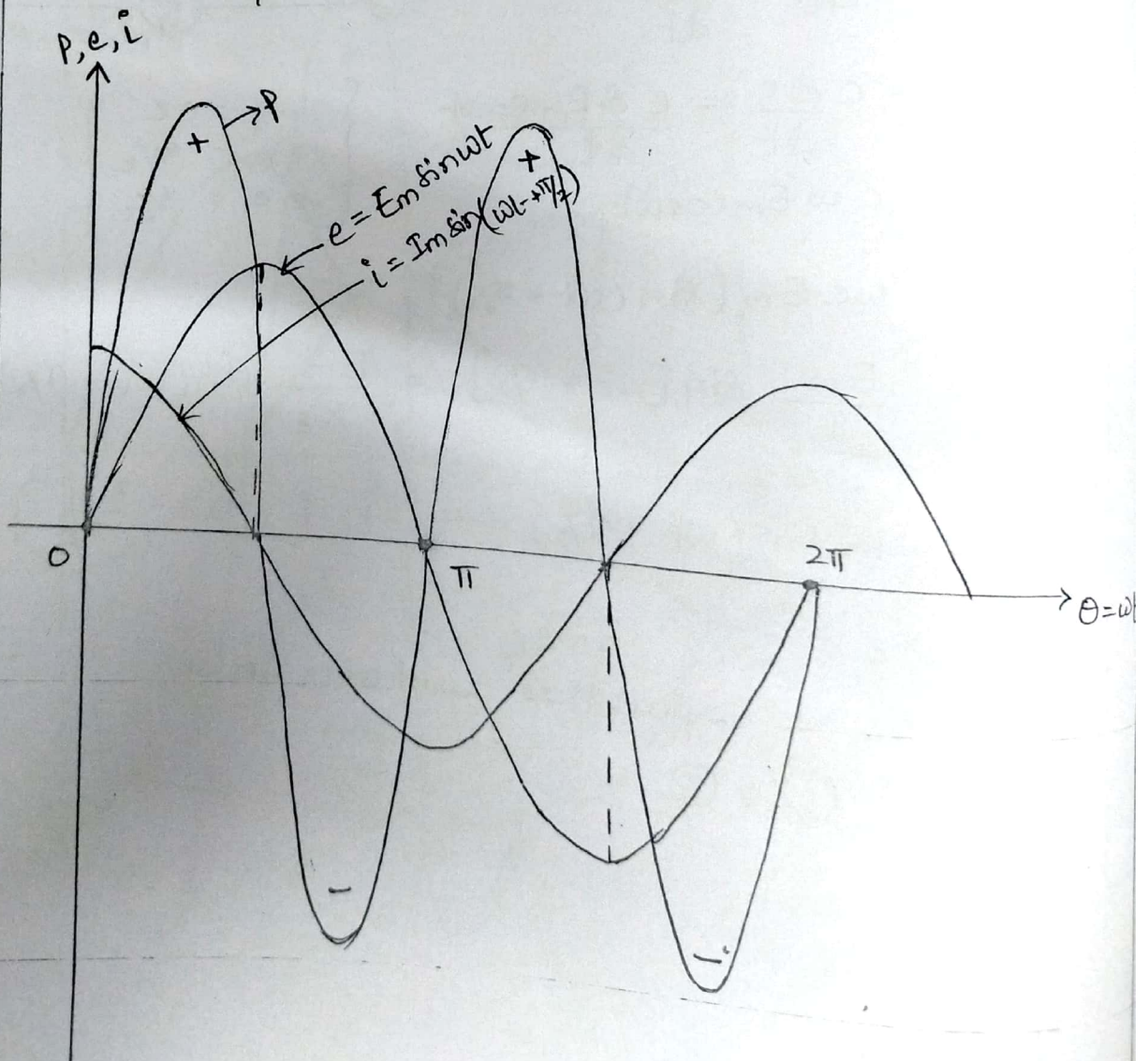

4) R-L Series circuit-

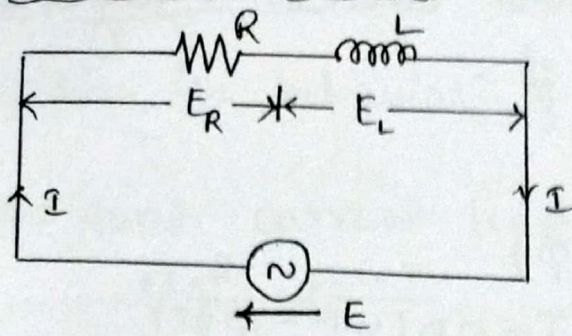


fig (1) circuit diagram

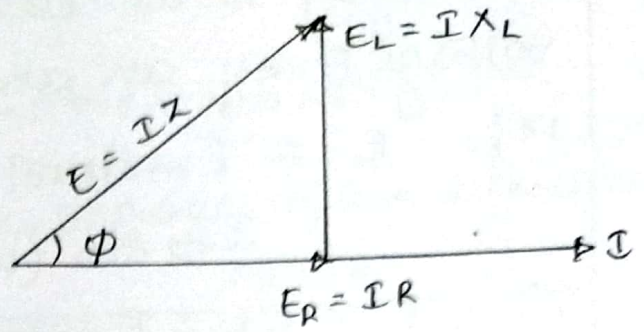


fig (2) vector diagram.

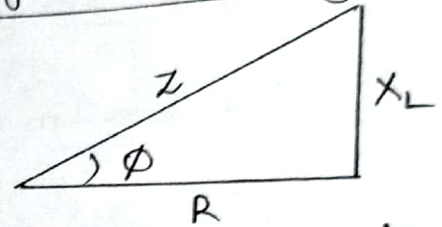


fig (3) Impedance triangle.

fig (2) shows the vector diagram where I is taken as the reference ('in series ckt c/t' is same). It consists of three voltages, $E_R = IR$ is in phase with the current, $E_L = IX_L$ leads the current by 90° .
 $E = IZ$ vector sum of E_R & E_L .

from fig (2)

$$E = IZ$$

$$I = \frac{E}{Z} \quad \text{--- (1)}$$

from fig (3)

$$Z = \sqrt{R^2 + X_L^2} \quad \text{--- (2)}$$

where ϕ is the power factor angle ϕ is given by.

$$\tan \phi = \frac{X_L}{R} \quad \phi \neq \tan$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right) \quad \text{--- (3)}$$

from fig (2) it is clear that current I lags the voltage E by an angle ϕ .

ie; $e = E_m \sin \omega t$

$i = I_m \sin (\omega t - \phi)$

$\therefore P = e i = E_m \sin \omega t \cdot I_m \sin (\omega t - \phi)$

$P = \frac{E_m I_m}{2} [\cos \phi - \cos (2\omega t - \phi)]$

$P = \frac{E_m I_m}{2} \cos \phi - \frac{E_m I_m}{2} \cos (2\omega t - \phi) \quad \text{--- (4)}$


In eqⁿ (4) the second term is

- *> Periodically varying quantity.
- *> Frequency is twice the supply frequency.
- *> The average power over a period is zero.

$\therefore P = \frac{E_m I_m}{2} \cos \phi = \frac{E_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$

$P = EI \cos \phi$

where $\cos \phi$ - Power factor.

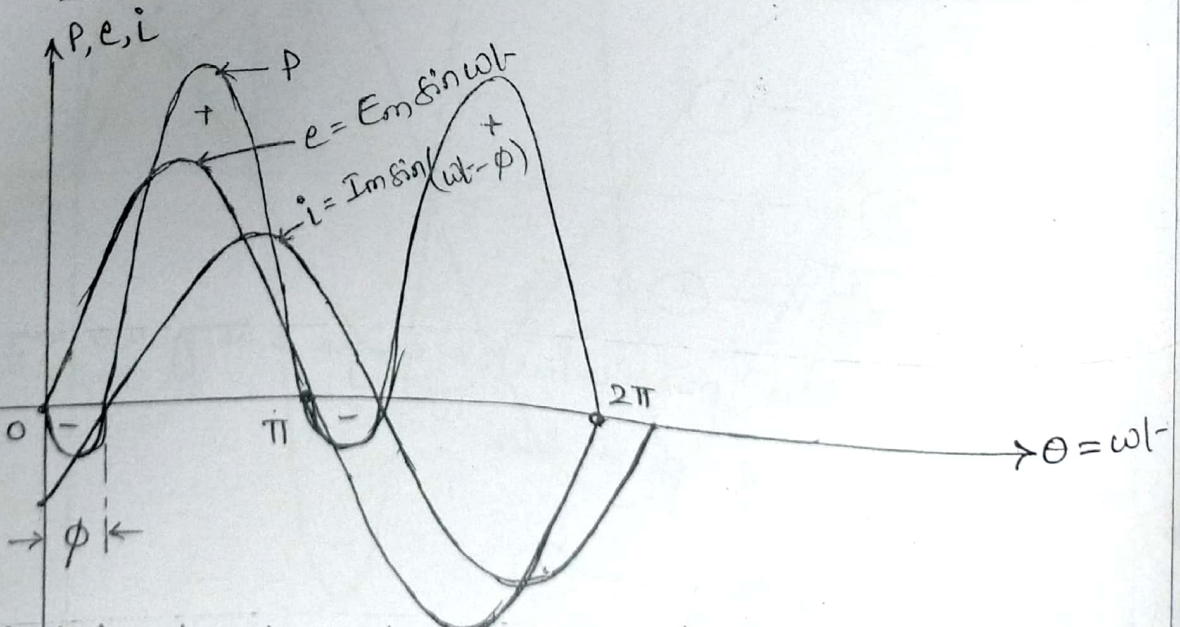

Explain the behavior of R-L Series circuit-

or

Show that current lags behind the voltage in R-L series circuit.

57) R-C series circuit:-

Q57) Explain the behavior of R-C series circuit.

or

Show that current leads the voltage in R-C series circuit

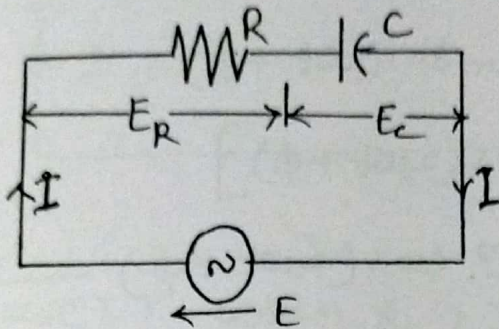


fig (1) circuit diagram

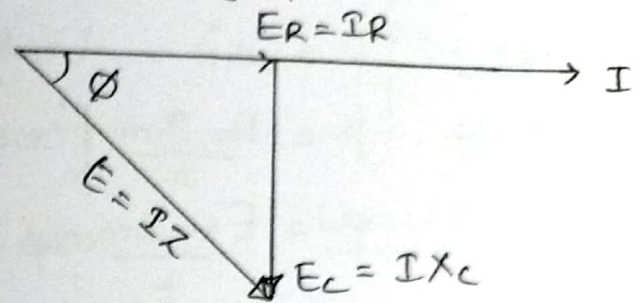


fig (2) Vector diagram

fig (2) shows the vector diagram where I is taken as the reference ($\because$ in series C & R is same). It consists of three

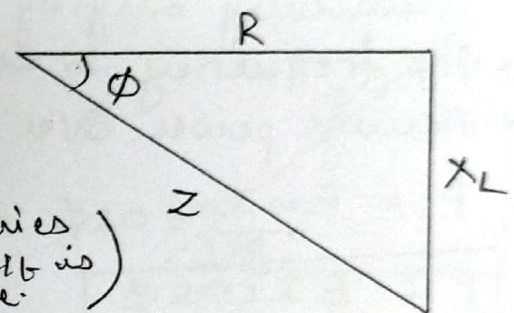


fig (3) Impedance triangle

voltages, $E = IR$

$E_R = IR$ is in phase with current

$E_C = IX_C$ lags the current by 90°

$E = IZ$ vector sum of E_R & E_C .

from fig (2)

$$E = IZ \quad \& \quad I = \frac{E}{Z} \quad \text{--- (1)}$$

from fig (3)

$$Z = \sqrt{R^2 + X_C^2} \quad \text{--- (2)}$$

where ϕ is the power factor angle is given by

$$\tan \phi = \frac{X_C}{R}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right) \quad \text{--- (3)}$$

from fig (2) it is clear that the current i leads the voltage e by an angle ϕ .

ie; $e = E_m \sin \omega t$

$i = I_m \sin(\omega t + \phi)$

Wkt:- $P = ei = E_m \sin \omega t \cdot I_m \sin(\omega t + \phi)$

$P = \frac{E_m I_m}{2} [\cos \phi - \cos(2\omega t + \phi)]$


$P = \frac{E_m I_m \cos \phi}{2} - \frac{E_m I_m \cos(2\omega t + \phi)}{2} \quad \text{--- (4)}$

In eqⁿ (4) the second term is

- *> Periodically varying quantity.
- *> Its frequency is twice the supply frequency
- *> Average power over a period is zero.

$\therefore P = \frac{E_m I_m \cos \phi}{2} = \frac{E_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$

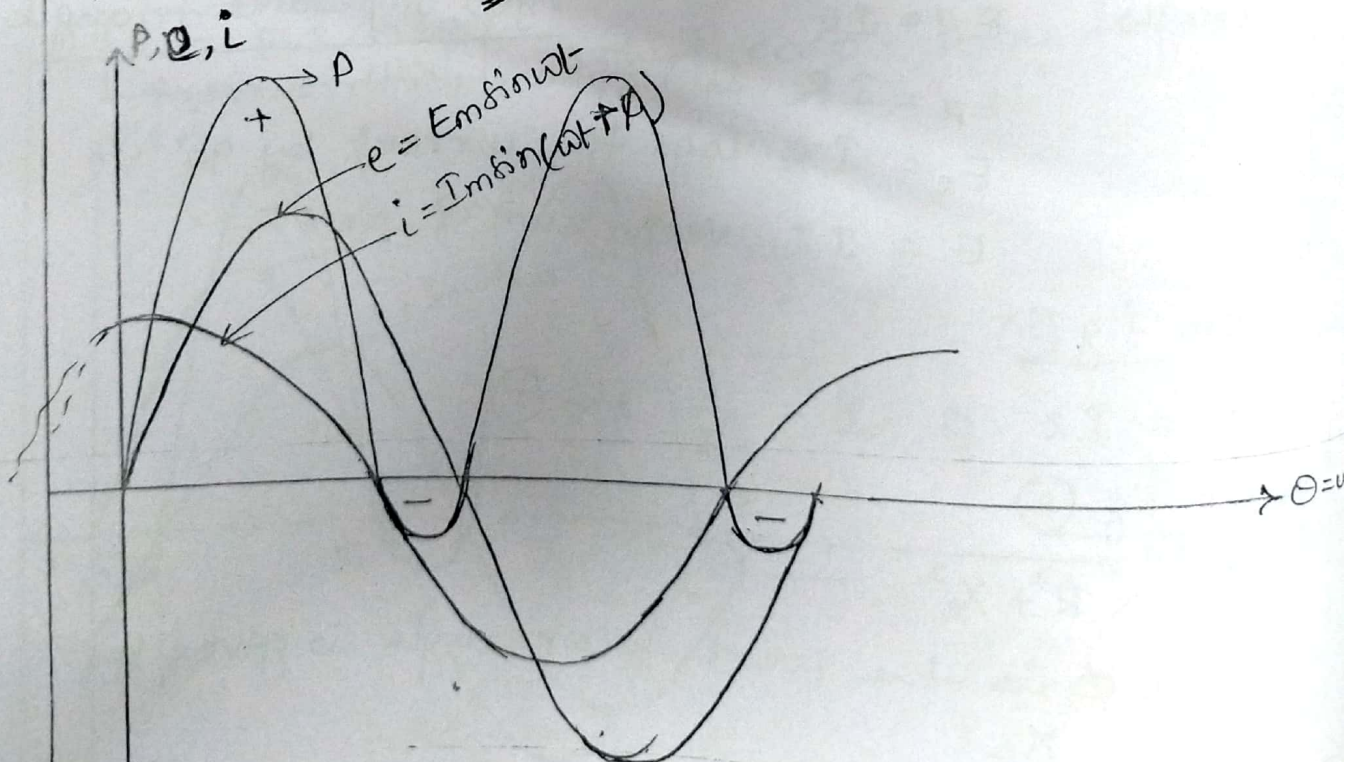$P = EI \cos \phi$ where $\cos \phi \rightarrow$ Power factor.



6) R-L-C Series circuit :- Q6) For a RLC series circuit discuss the nature of Power factor i) $X_L > X_C$
 ii) $X_L < X_C$
 iii) $X_L = X_C$

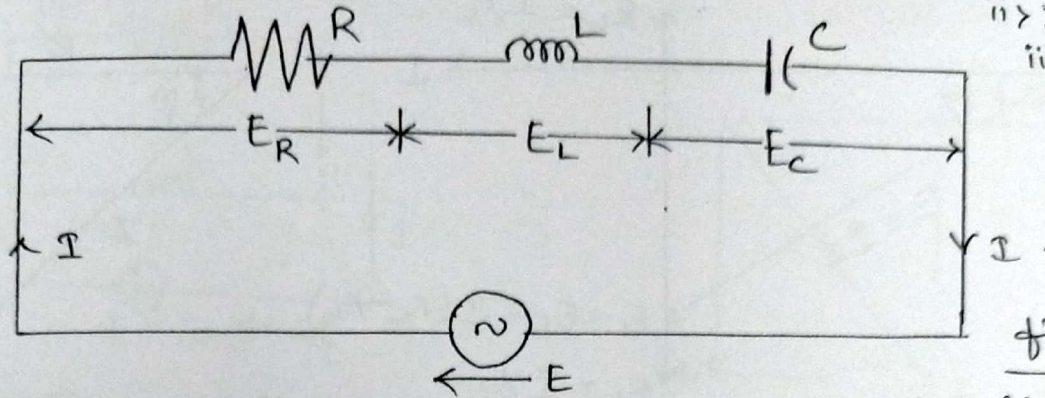


fig ①

Circuit diagram

Case 1 :- when $X_L > X_C$.

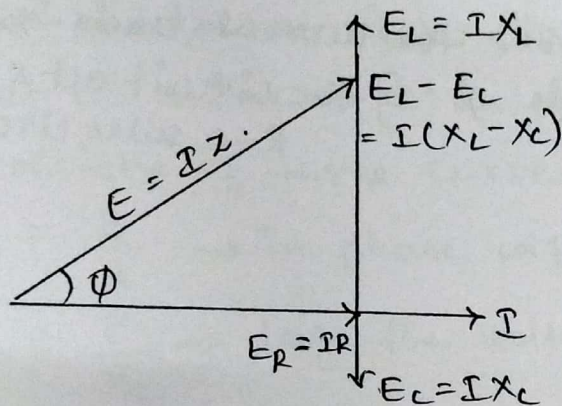


fig ② Vector diagram

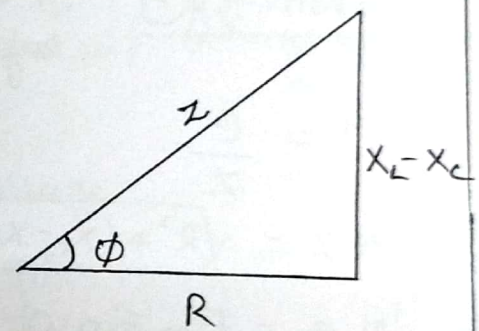


fig ③ Impedance Δ

From fig ② : $\Rightarrow$ It is clear that the current lags the voltage by an angle ϕ & circuit acts as R-L series circuit

$$I = \frac{E}{Z}$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V e = E_m \sin \omega t$$


$$\text{then } i = I_m \sin (\omega t - \phi)$$

$$\therefore P = EI \cos \phi$$

case 2 :- when $X_C > X_L$

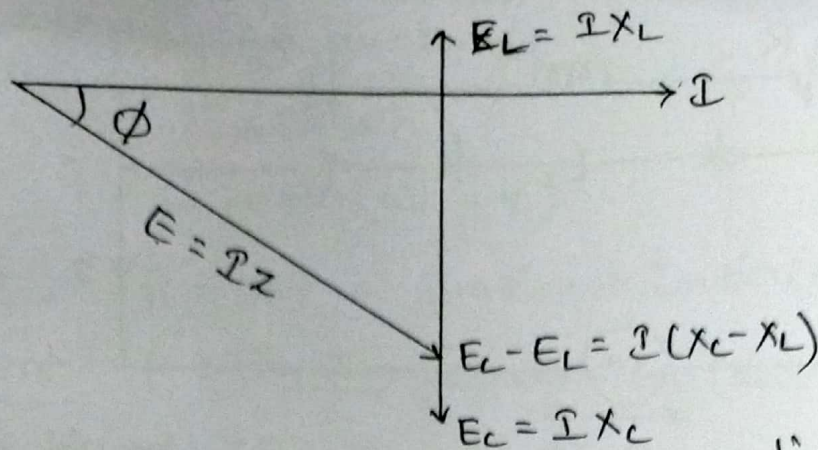

fig(4) vector diagram

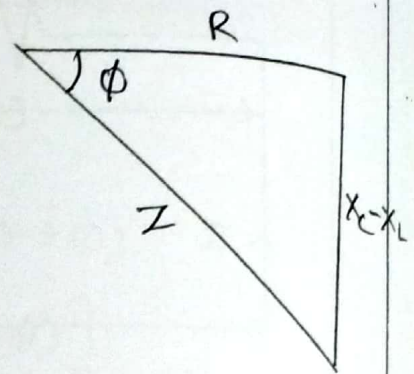

fig(5) Impedance triangle

from fig(2) :- It is clear that the current leads the voltage by an angle ϕ the circuit acts as R-C series circuit.

$$I = \frac{E}{Z}$$


$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$e = E_m \sin \omega t$$

$$\text{then } i = I_m \sin(\omega t - \phi)$$

$$\therefore P = EI \cos \phi$$

case 3 :- when $X_L = X_C$

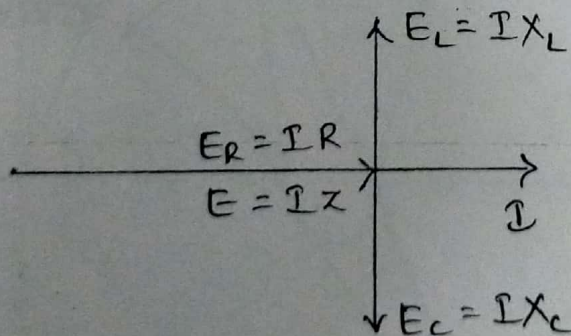

when $X_L = X_C$ then E_L & E_C cancel each other and the circuit acts as pure R-circuit hence current I is in phase with voltage E .

$$\therefore Z = R$$

$$E_R = IR$$

$$E = IZ$$

$$\text{If } e = E_m \sin \omega t \text{ then } i = I_m \sin \omega t$$

$$\therefore P = EI$$

8) Power and Power Triangle

- Q.1) Draw the power triangle and define i) Real power
ii) Reactive power iii) Apparent power.


Wkt $P = VI \cos \phi$ watts.

$\Phi \quad V = V_R + V_L$

Multiply both sides by I

$\therefore VI = V_R I + V_L I = V \cos \phi I + V \sin \phi I$

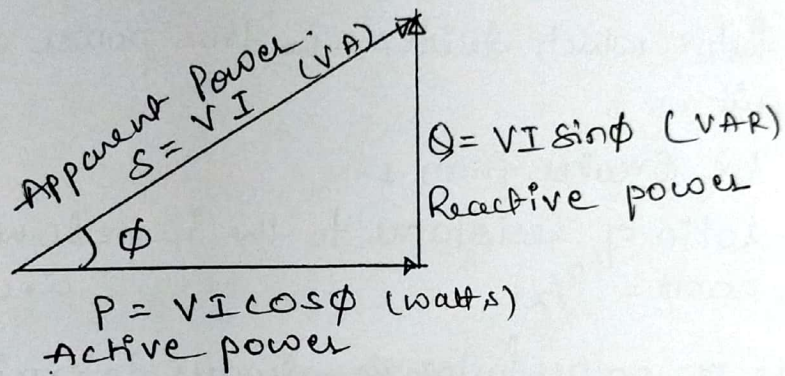From this equation the power triangle can be obtained as:



- i) Real power $\equiv$ Active power (P) :-

It is the product of applied voltage and the active component of the current.

ie; $P = VI \cos \phi$ watts.

- ii) Reactive Power (Q) :-

It is the product of applied voltage and the reactive component of the current.

ie; $Q = VI \sin \phi$ VAR.

- iii) Apparent power $\equiv$ Total power (S) :-

It is the product of the rms values of voltage and current.

ie; $S = VI$ VA.

Q7 Power factor :

Q8 Define power factor and explain its significance in AC circuit.

It is the ratio of true power to apparent power.

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}} = \frac{VI \cos \phi}{VI} = \cos \phi$$

or It is the cosine angle between voltage and current.

Significance of power factor in a.c circuit :

* It is the factor which decides the true power consumption in the circuit.

* It cannot be greater than 1.

* It is the ratio of resistance to the impedance of the circuit.
i.e; $\cos \phi = R/Z$.

*

* The nature of power factor is always determined by position of current with respect to the voltage.

* If current lags voltage then the power factor is said to be lagging and the inductive loads have the lagging power factor.

* If current leads voltage then the power factor is said to be leading and the capacitive loads have the leading power factor.

* So, for pure inductance, the power factor is $\cos(90^\circ) = 0$ i.e; zero lagging. While for pure capacitance, the power factor is $\cos(90^\circ) = 0$ but leading.


* For a pure resistive circuit the voltage and current are in phase hence the power factor $\cos(0^\circ) = 1$ i.e; unity power factor.

∴ Numericals of ϕ AC circuit :-

- Ex ① A circuit consists of a resistance of 20Ω , an inductance of $0.05H$ connected in series. A supply of $230V$ at $50Hz$ is applied across the circuit. Find
i) Current ii) power factor iii) power consumed by the circuit
iv) Voltage drop across R & L v) Draw the vector diagram.

Solⁿ :-

Given :- $R = 20\Omega$ $L = 0.05H$

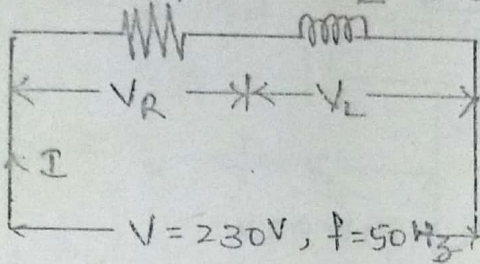

Find :- i) $I = ?$

ii) $P.f = \cos \phi = ?$

iii) $P = ?$

iv) V_R & $V_L = ?$

i) Wkt :- $I = \frac{V}{Z}$ — (1)

Wkt :- $Z = \sqrt{R^2 + X_L^2}$ — (2)

Wkt :- $X_L = 2\pi f L = 2\pi \times 50 \times 0.05 = 15.7\Omega$

∴ (2) $\Rightarrow Z = \sqrt{(20)^2 + (15.7)^2} = 25.42\Omega$

∴ (1) $\Rightarrow I = \frac{230}{25.42} = 9.04A$

$I = 9.04A$

ii) Wkt :- $P.f = \cos \phi = \frac{R}{Z} = \frac{20}{25.42} = 0.786$

$P.f = \cos \phi = 0.786$ (lagging)

iii) Wkt :- $P = VI \cos \phi = 230 \times 9.04 \times 0.786$

$P = 1634.43 \text{ watts}$


iv) WKA $\therefore V_R = I R = 9.04 \times 20 = 180.8 \text{ V}$

$$V_R = 180.8 \text{ Volts}$$

WKA $\therefore V_L = I X_L = 9.04 \times 15.7 = 141.92 \text{ V}$

$$V_L = 141.92 \text{ Volts.}$$

v) Phasor / Vector diagram

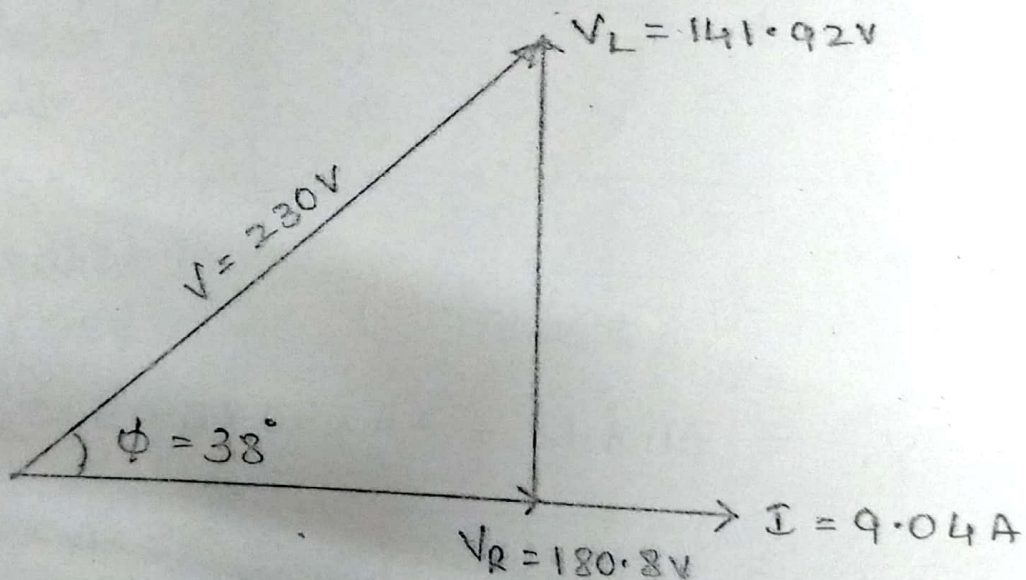

WKA $\therefore \cos \phi = 0.786$


$$\phi = \cos^{-1}(0.786)$$

$$\phi = 38^\circ$$

Ex ② A circuit consists of a resistance of 25Ω and a capacitance of $100\mu\text{F}$ connected in series. A supply of 200V , 50Hz is applied across the circuit. Find
 i) Impedance ii) Current iii) power factor iv) power
 v) Voltage drop across R & C vi) Vector diagram.

Soln:-

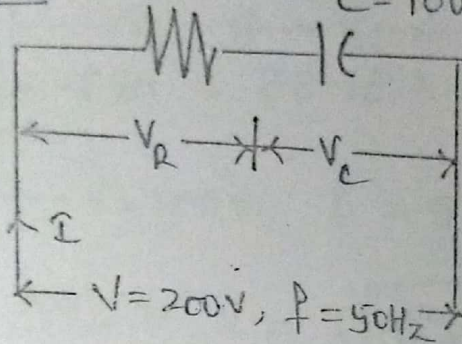Given:- $R = 25\Omega$ $C = 100 \times 10^{-6}\text{F}$



Find:- i) $Z = ?$

ii) $I = ?$

iii) $\text{p.f} = \cos\phi = ?$

iv) $P = ?$

v) V_R & $V_C = ?$

i) Wkt:- $Z = \sqrt{R^2 + X_C^2}$ — (1)

Wkt:- $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = \frac{10^6}{100\pi \times 100}$

$X_C = 31.85\Omega$

$\therefore$ (1) $\Rightarrow Z = \sqrt{(25)^2 + (31.85)^2} = 40.48\Omega$

$Z = 40.48\Omega$

ii) Wkt:- $I = \frac{V}{Z} = \frac{200}{40.48} = 4.94\text{A}$

$I = 4.94\text{A}$

iii) Wkt:- $\text{p.f} = \cos\phi = \frac{R}{Z} = \frac{25}{40.48} = 0.617 \text{ leading}$

$\text{p.f} = \cos\phi = 0.617 \text{ leading}$

iv) work: $P = VI \cos \phi = 200 \times 4.94 \times 0.617$

$$P = 609.59 \text{ watts}$$


v) work: $V_R = IR = 4.94 \times 25 = 123.5 \text{ V}$

$$V_R = 123.5 \text{ V}$$

work: $V_C = I X_C = 4.94 \times 31.85 = 157.34 \text{ V}$

$$V_C = 157.34 \text{ V}$$

vi) Phasor diagram:-

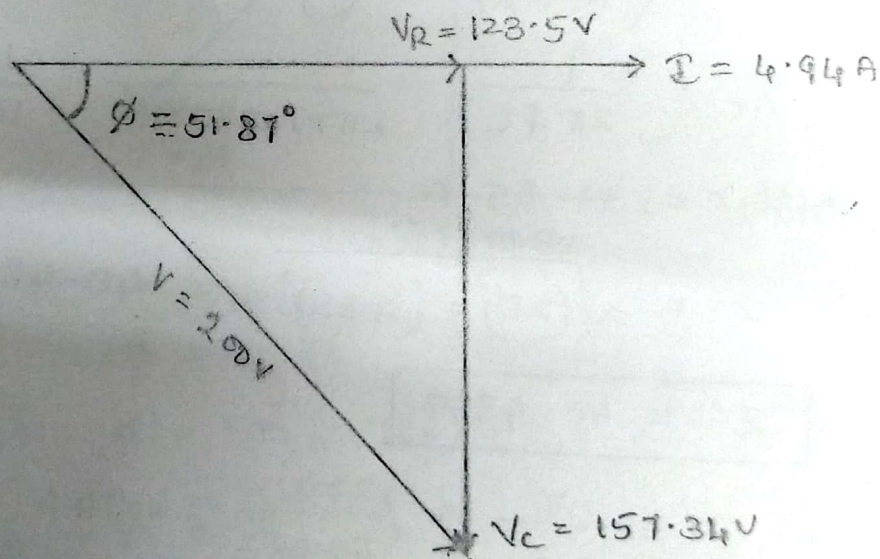

work:- $\cos \phi = 0.617$


$$\therefore \phi = \cos^{-1}(0.617)$$

$$\phi = 51.87^\circ$$

Ex ③ A circuit consists of a resistance of 10Ω an inductance of 16mH & a capacitance of $150\mu\text{F}$ connected in series. A supply of 100V at 50Hz is given to the circuit. Find
 i) Impedance ii) Current iii) power factor iv) power
 v) Voltage drop across R, L & C vi) Draw phasor diagram

Solⁿ:

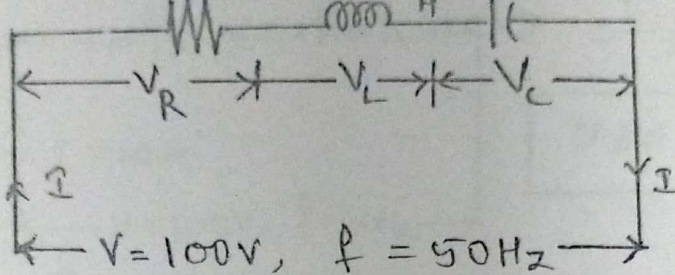Given: $R = 10\Omega$ $L = 16 \times 10^{-3}\text{H}$ $C = 150 \times 10^{-6}\text{F}$



Find:- i) $Z = ?$

ii) $I = ?$

iii) P.f. = $\cos\phi = ?$

iv) $P = ?$

v) $V_R, V_L \& V_C = ?$

i) Wkt:- $Z = \sqrt{R^2 + (X_L - X_C)^2}$ $\therefore Z = \sqrt{R^2 + (X_C - X_L)^2}$

$\therefore$ Wkt:- $X_L = 2\pi f L = 2\pi \times 50 \times 16 \times 10^{-3} = 5.024\Omega$

Wkt:- $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 150 \times 10^{-6}} = 21.23\Omega$

ie; $X_C > X_L$

$\therefore Z = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{10^2 + (21.23 - 5.024)^2}$

$$Z = 19.04\Omega$$

ii) Wkt:- $I = \frac{V}{Z} = \frac{100}{19.04} = 5.25\text{A}$

$$I = 5.25\text{A}$$

iii) Wkt:- P.f. = $\cos\phi = \frac{R}{Z} = \frac{10}{19.04} = 0.525$

$$\text{P.f.} = 0.525 \text{ (leading)}$$

iv) Wkt:- $P = VI \cos\phi = 100 \times 5.25 \times 0.525$

$$P = 275.625 \text{ watts}$$

v) Wkt :- $V_R = IR = 5.25 \times 10 = 52.5 \text{ V}$

Wkt :- $V_R = 52.5 \text{ V}$


Wkt :- $V_L = IX_L = 5.25 \times 5.024 = 26.38 \text{ V}$

$V_L = 26.38 \text{ V}$

Wkt :- $V_C = IX_C = 5.25 \times 21.23 = 111.46 \text{ V}$

$V_C = 111.46 \text{ V}$

vi) Phasor diagram :-

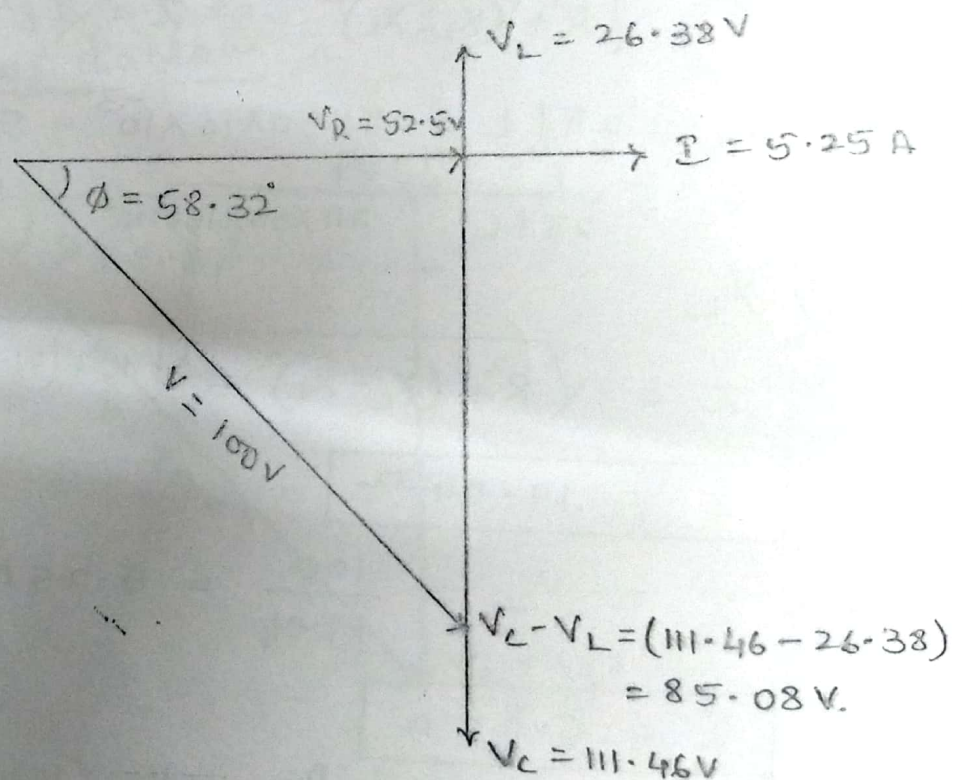


Wkt :- $\cos \phi = 0.525$

$\therefore \phi = \cos^{-1}(0.525)$

$\phi = 58.32^\circ$

- Ex (4) An inductive coil takes a current of 10 A from a supply of 100 V, 50 Hz and it lags the voltage by 30° . Calculate
- parameters of the circuit.
 - Power factor
 - Active power, reactive power and apparent power.

Solⁿ: Given:- $R = ?$ $L = ?$

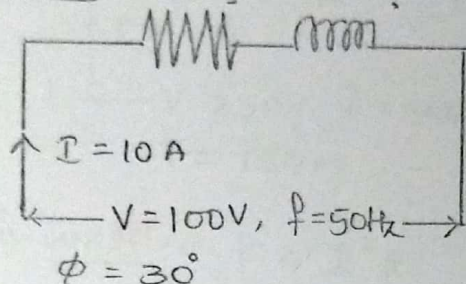

Find:- i) R & $L = ?$

ii) P.f = $\cos \phi = ?$

iii) $P = ?$, $Q = ?$ & $S = ?$

i) Wkt:- $Z = \frac{V}{I} = \frac{100}{10} = 10 \Omega$

Wkt:- $R = Z \cos \phi = 10 \cos(30) = 8.66 \Omega$

$$R = 8.66 \Omega$$

Wkt:- $X_L = Z \sin \phi = 10 \sin(30) = 5 \Omega$

Wkt:- $X_L = 2\pi f L$

Wkt:- $L = \frac{X_L}{2\pi f} = \frac{5}{2\pi \times 50} = 0.0159 \text{ H}$

$$L = 0.0159 \text{ H}$$

ii) Wkt:- P.f = $\cos \phi = \cos(30) = 0.866$


$$\text{P.f} = 0.866 \text{ lagging}$$

iii) Active power $P = VI \cos \phi = 100 \times 10 \times 0.866 = 866 \text{ Watts}$

Reactive power $Q = VI \sin \phi = 100 \times 10 \times 0.5 = 500 \text{ VAR}$

Apparent Power $S = VI = 100 \times 10 = 1000 \text{ VA}$

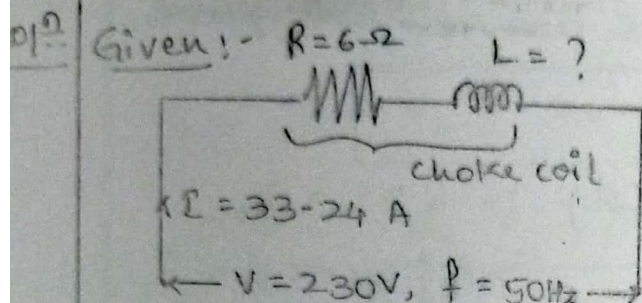25) An inductive coil takes a current of 33.24 A from 230V, 50Hz supply. If the resistance of the coil is 6Ω , calculate the inductance of the coil and the power taken by the coil.



Find:- i) $L = ?$
ii) $P = ?$

i) Wkt $X_L = 2\pi fL$

$\therefore L = \frac{X_L}{2\pi f} \quad \text{--- (1)}$

Wkt:- $Z = \sqrt{R^2 + X_L^2}$

$\therefore X_L = \sqrt{Z^2 - R^2} \quad \text{--- (2)}$

Wkt:- $Z = \frac{V}{I} = \frac{230}{33.24} = 6.92\Omega$

$\therefore \text{(2)} \Rightarrow X_L = \sqrt{(6.92)^2 - (6)^2} = 3.45\Omega$

$\text{(1)} \Rightarrow L = \frac{3.45}{2\pi \times 50} = 0.01098\text{ H}$

$L = 0.01098\text{ H}$

ii) Wkt:- $P = I^2 R = (33.24)^2 \times 6$


$P = 6629.38\text{ watt}$

Note:- In a choke coil ie; R-L series circuit only the R component ie; Resistance consumes the power hence $P = I^2 R$

Ex ⑥ An inductive coil is connected to supply of 250V at 50Hz and takes a current of 5A. The coil dissipates 750W calculate power factor, resistance and inductance of the coil.

Soln.

Given :- $R = ?$ $L = ?$

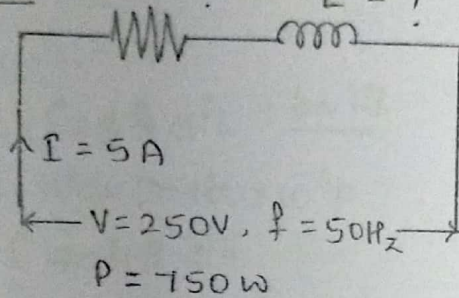

Find :- i) $R = ?$

ii) $L = ?$

iii) P.f = ?

i) Wkt :- $P = I^2 R$

$$\therefore R = \frac{P}{I^2} = \frac{750}{(5)^2} = 30 \Omega$$

$$\boxed{R = 30 \Omega}$$

ii) Wkt :- $X_L = 2\pi f L$

$$L = \frac{X_L}{2\pi f} \quad \text{--- (1)}$$

Wkt :- $Z = \sqrt{R^2 + X_L^2}$

$$\therefore X_L = \sqrt{Z^2 - R^2} \quad \text{--- (2)}$$

Wkt :- $Z = \frac{V}{I} = \frac{250}{5} = 50 \Omega$

$$\therefore \textcircled{2} \Rightarrow X_L = \sqrt{(50)^2 - (30)^2} = 40 \Omega$$

$$\therefore \textcircled{1} \Rightarrow L = \frac{40}{2\pi \times 50} = 127.32 \times 10^{-3} \text{ H}$$


$$\boxed{L = 127.32 \text{ mH}}$$

iii) Wkt :- $\text{P.f} = \cos \phi = \frac{R}{Z} = \frac{30}{50} = 0.6$

$$\boxed{\text{P.f} = 0.6 \text{ lagging}}$$

Ex 7) A 125V, 60Hz is applied across a capacitance connected in series with a non-inductive resistor. The combination carries a current of 2.2 A and consumes a power of 96.8 watts. Calculate the R & C of the circuit and P.f of the circuit.

Sol:

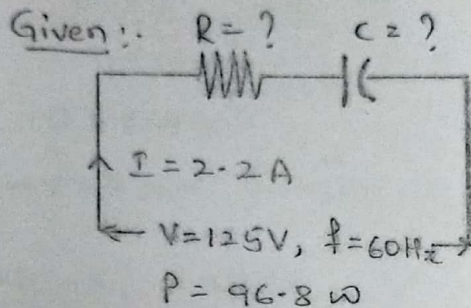

Find: i) $R = ?$
 ii) $C = ?$
 iii) P.f = ?

i) Wkt: $P = I^2 R$

$$\therefore R = \frac{P}{I^2} = \frac{96.8}{(2.2)^2} = 20 \Omega$$

$$R = 20 \Omega$$

ii) Wkt: $X_C = \frac{1}{2\pi f C}$

$$\therefore C = \frac{1}{2\pi f X_C} \quad \text{--- (1)}$$

Wkt: $Z = \sqrt{R^2 + X_C^2}$

$$\therefore X_C = \sqrt{Z^2 - R^2} \quad \text{--- (2)}$$

Wkt: $Z = \frac{V}{I} = \frac{125}{2.2} = 56.81 \Omega$

$$\therefore \text{(2)} \Rightarrow X_C = \sqrt{(56.81)^2 - (20)^2} = 53.18 \Omega$$

$$\text{(1)} \Rightarrow C = \frac{1}{2\pi \times 60 \times 53.18} = 4.98 \times 10^{-5} \text{ F}$$

$$C = 49.8 \mu\text{F} \approx 50 \mu\text{F}$$

iii) Wkt: $\text{P.f} = \cos \phi = \frac{R}{Z} = \frac{20}{56.81} = 0.352 \text{ leading}$

Ex ⑧ A coil of power factor 0.6 is in series with a $100\mu\text{F}$ capacitor. When connected to a 50Hz supply, the potential difference across the coil is equal to the potential difference across the capacitor. Find the resistance and inductance of the coil.

Sol.

Given:-


$$\text{P.f} = \cos\phi = 0.6$$

$$C = 100\mu\text{F} = 100 \times 10^{-6}\text{F}$$

$$f = 50\text{Hz}$$

$$V_Z = V_C$$

Find:- R & $L = ?$

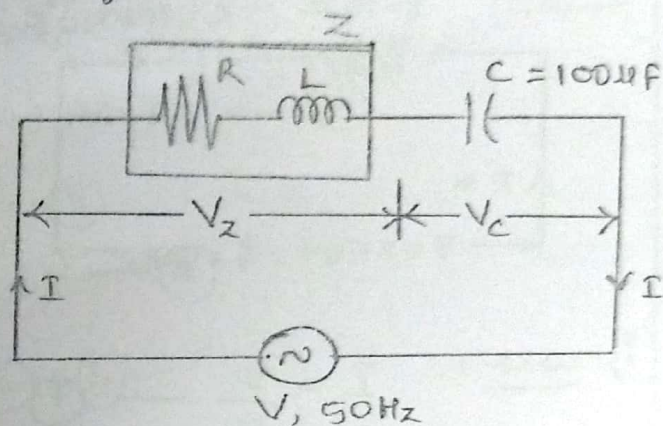

Given that $V_Z = V_C$

$$Z = X_C$$

$$Z = X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$Z = 31.83\Omega$$

Wkt:- $R = Z \cos\phi = 31.83 \times 0.6 = 19.098\Omega$

$$R = 19.098\Omega$$

Wkt:- $X_L = Z \sin\phi = 31.83 \sin[\cos^{-1}(0.6)] = 25.46\Omega$


Wkt:- $X_L = 2\pi f L$

$$\therefore L = \frac{X_L}{2\pi f} = \frac{25.46}{2\pi \times 50} = 0.081\text{H}$$

$$L = 0.081\text{H}$$

Ex 9) A non-inductive resistor of 10Ω is in series with a capacitor of $100\mu\text{F}$ across a $250\text{V}/50\text{Hz}$ supply. Determine the current taken by the capacitor and power factor of the circuit.

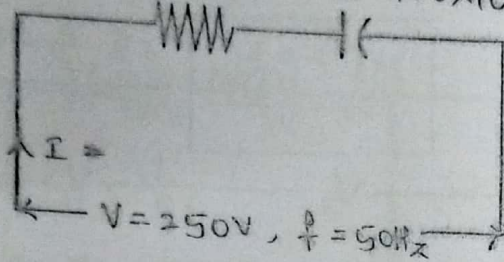Solⁿ Given:- $R = 10\Omega$ $C = 100 \times 10^{-6}\text{F}$



Find:- i) $I = ?$

ii) $\text{P.f} = \cos\phi = ?$

i) Wkt:- $I = \frac{V}{Z}$ — (1)

Wkt:- $Z = \sqrt{R^2 + X_c^2}$ — (2)

Wkt:- $X_c = \frac{1}{2\pi f C} = \frac{10^6}{2\pi \times 50 \times 100} = 31.83\Omega$

$\therefore$ (2) $\Rightarrow Z = \sqrt{(10)^2 + (31.83)^2} = 33.36\Omega$

$\therefore$ (1) $\Rightarrow I = \frac{250}{33.36} = 7.493\text{A}$

$I = 7.49\text{A}$

ii) Wkt:- $\text{P.f} = \cos\phi = \frac{R}{Z} = \frac{10}{33.36} = 0.299 \approx 0.3$

$\text{P.f} = \cos\phi = 0.3 \text{ leading}$

Ex 10) Given $v = 200 \sin 377t$ volts and $i = 8 \sin (377t - 30^\circ)$ Amps for an a.c circuit. determine.
 i) power factor ii) True power iii) Apparent power
 iv) Reactive power. Indicate the unit of power calculated.

Sol: Given :- $v = (200 \sin 377t)$ volts — (1)

$i = 8 \sin (377t - 30^\circ)$ Amps — (2)

Wkt :- $v = V_m \sin \omega t$ — (3)

$i = I_m \sin (\omega t - \phi)$ — (4)

compare (1) & (3) and (2) & (4).

we get $V_m = 200 \text{ V}$, $I_m = 8 \text{ A}$, $\phi = 30^\circ$ & $\omega = 377$.

Wkt :- $V = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.42 \text{ Volts}$.

Wkt :- $I = \frac{I_m}{\sqrt{2}} = \frac{8}{\sqrt{2}} = 5.656 \text{ Amps}$.

Wkt :- $\omega = 2\pi f = 377$

$\therefore f = \frac{377}{2\pi} = 60 \text{ Hz}$

i) Wkt $P.f = \cos \phi = \cos (-30^\circ) = 0.866$

$P.f = 0.866$ (lagging)

ii) Wkt $P = VI \cos \phi = 141.42 \times 5.656 \times 0.866$

$P = 692.8 \text{ Watts}$

iii) Wkt $S = VI = 141.42 \times 5.656$

$S = 799.87 \text{ VA}$

iv) Wkt $Q = VI \sin \phi = 141.42 \times 5.656 \times \sin (30^\circ)$

$Q = 399.93 \text{ VAR} \approx 400 \text{ VAR}$

22 (11) An emf whose instantaneous value is $100 \sin(314t - \pi/4)$ V is applied to a circuit and the current flowing through it is $20 \sin(314t - 1.5708)$ A. Find the frequency and the values of circuit elements assuming series combination of circuit elements.

Solⁿ:- Given :- $V = 100 \sin(314t - \pi/4)$ V $= 100 \sin(314t - 45^\circ)$ V — (1)
 $i = 20 \sin(314t - 1.5708)$ A $= 20 \sin(314t - 90^\circ)$ A — (2)

Wkt :- $V = V_m \sin(\omega t - \phi_1)$ — (3)

$i = I_m \sin(\omega t - \phi_2)$ — (4)

Note :- $\pi \text{ rad} = 180^\circ$
 $1.5708 \text{ rad} = ?$
 $\therefore \frac{1.5708 \times 180}{\pi} = 90^\circ$

Compare (1) with (3) & (2) with (4)

We get $V_m = 100$ V, $I_m = 20$ A, $\phi = \phi_1 - \phi_2 = 45^\circ - (-90^\circ)$
 $\phi = 45^\circ$

i) Wkt :- $\omega = 2\pi f = 314$

$\therefore f = \frac{314}{2\pi}$ ~~2144~~

$f = 50 \text{ Hz}$

ii) Wkt :- $V = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71$ V $= 70.71 \angle -45^\circ$

Wkt :- $I = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.142$ A $= 14.142 \angle -90^\circ$

Wkt :- $Z = \frac{V}{I} = \frac{70.71 \angle -45^\circ}{14.142 \angle -90^\circ} = 5 \angle 45^\circ + 90^\circ$

$Z = 5 \angle 45^\circ \Omega = 3.5355 + j 3.5355 \Omega$

Wkt :- $Z = R + jX_L$ — (5)

compare (5) & (6)

$R = 3.5355 \Omega$

$X_L = 3.5355 \Omega = 2\pi f L$

$L = \frac{X_L}{2\pi f} = \frac{3.5355}{2\pi \times 50}$

$L = 11.25 \text{ mH}$

Ex 12

An ac voltage of $100 \sin(314t + 60^\circ) \text{ V}$ is applied to a circuit which carries a current of $20 \sin(314t + 30^\circ) \text{ A}$. Calculate
 i) rms values of voltage and current.
 ii) Impedance iii) Power factor iv) Active, reactive & apparent power.

Soln:

Given:- $V = 100 \sin(314t + 60^\circ) \text{ V}$ — (1)

$I = 20 \sin(314t + 30^\circ) \text{ A}$ — (2)

find:- i) $V_{\text{rms}} = V = ?$ iii) $\text{P.f} = \cos \phi = ?$

ii) $Z = ?$ iv) $I_{\text{rms}} = I = ?$ v) $P, Q \text{ \& } S = ?$

Wkt:- $V = V_m \sin(\omega t + \phi_1) \text{ V}$ — (3)

$I = I_m \sin(\omega t + \phi_2) \text{ A}$ — (4)

Compare (1) & (3) and (2) & (4).

we get:- $V_m = 100 \text{ V}$, $I_m = 20 \text{ A}$, $\omega = 314 = 2\pi f$.

$\therefore f = \frac{314}{2\pi} = 50 \text{ Hz}$.

i) Wkt:- $V_{\text{rms}} = V = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71 \text{ V}$

$V = 70.71 \text{ V}$ or $V = 70.71 \angle 60^\circ$

Wkt:- $I_{\text{rms}} = I = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.14 \text{ A}$

$I = 14.14 \text{ A}$ or $I = 14.14 \angle 30^\circ$

ii) Wkt:- $Z = \frac{V}{I} = \frac{70.71 \angle 60^\circ}{14.14 \angle 30^\circ} = 5 \angle 30^\circ \Omega$

$Z = 5 \angle 30^\circ \Omega = 4.33 + j2.5 \Omega$ — (5)

Wkt:- $Z = R + jX_L$ — (6)

compare (5) & (6) we get

$R = 4.33 \Omega$

$$X_L = 2.5 \Omega$$

Wkt :- $X_L = 2\pi fL$

$$\therefore L = \frac{X_L}{2\pi f} = \frac{2.5}{2\pi \times 50} = 7.95 \times 10^{-3} \text{ H}$$

$$L = 7.95 \text{ mH}$$

iv) Power Wkt :- $P.f = \cos \phi = \frac{R}{Z} = \frac{4.33}{5} = 0.866$ lagging

or Wkt :- $P.f = \cos 30^\circ = 0.866$ lagging

v) Wkt :- $P = VI \cos \phi = 70.71 \times 14.14 \times 0.866$

$$P = 865.86 \text{ Watts}$$

Wkt :- $Q = VI \sin \phi = 70.71 \times 14.14 \times \sin(30^\circ)$

$$Q = 499.91 \text{ VAR} \approx 500 \text{ VAR}$$

Wkt :- $S = VI = 70.71 \times 14.14$

$$S = 999.839 \text{ VA} \approx 1000 \text{ VA}$$

Ex (13) A single phase AC series circuit has an emf of $100 \cos(314t - 60^\circ) \text{ V}$ and current of $20 \sin(314t - 0.5) \text{ A}$. Find the parameters of the circuit.

Solⁿ: Given: $V = 100 \cos(314t - 60^\circ) \text{ V}$ & $I = 20 \sin(314t - 0.5) \text{ A}$

Wkt:- $V = 100 \sin(314t - 60^\circ + 90^\circ) \text{ V} = 100 \sin(314t + 30^\circ) \text{ V}$

Wkt:- $I = 20 \sin(314t - 28.647^\circ) \text{ A}$ — (1)

Wkt:- $V = V_m \sin(\omega t + \phi_1)$ — (3)

& $I = I_m \sin(\omega t - \phi_2)$ — (4)

Compare (1) & (2) and (3) & (4)

We get:- $V_m = 100 \text{ V}$, $I_m = 20 \text{ A}$, $\omega = 314 = 2\pi f$

$$\therefore f = \frac{314}{2\pi} = 50 \text{ Hz}$$

Parameters of the circuit:-

$$\text{Wkt:- } I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.14 \text{ A}$$

$$\text{Wkt:- } V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71 \text{ V}$$

but ϕ_1 and ϕ_2 can be written in polar form.

$$\text{ie; } I = 14.14 \angle -28.647^\circ \text{ A} \quad \& \quad V = 70.71 \angle 30^\circ \text{ V}$$

$$\text{Wkt:- } Z = \frac{V}{I} = \frac{70.71 \angle 30^\circ}{14.14 \angle -28.647^\circ} = 5 \angle 30 + 28.647$$

$$Z = 5 \angle 58.647^\circ \Omega = 2.6 + j4.269 \Omega \text{ — (5)}$$

$$\text{Wkt:- } Z = R + jX_L \text{ — (6)}$$

Compare (5) & (6) we get:

$$R = 2.6 \Omega \quad \& \quad X_L = 4.269 \Omega$$

WkP :- $X_L = 2\pi fL$

$$L = \frac{X_L}{2\pi f} = \frac{4.269}{2\pi \times 50} = 0.01354$$

$$L = 0.01354 \text{ H}$$

∴ the parameters of the circuit are

$R = 2.6 \Omega$
\$ $L = 0.01354$

- Ex (14) A single phase voltage of $(160 + j120) \text{ V}$ is applied across a circuit which carries a current of $(6 + j8) \text{ A}$. Draw the vector diagram and find.
- The elements of the circuit when the frequency is 50 Hz .
 - power factor of the circuit.
 - Power consumed by the circuit.

Soln

Given: $V = (160 + j120) \text{ V} = 200 \angle 36.86^\circ \text{ V}$

$I = (6 + j8) \text{ A} = 10 \angle 53.13^\circ \text{ A}$

i) Elements of the ckt

Wkt: $Z = \frac{V}{I} = \frac{200 \angle 36.86^\circ}{10 \angle 53.13^\circ} = 20 \angle 36.86^\circ - 53.13^\circ$

$Z = 20 \angle -16.27^\circ = 19.19 - j5.6 \Omega$ — (1)

Wkt: $Z = R - jX_C$ — (2)

compare (1) & (2) we get

$R = 19.19 \Omega$

$X_C = 5.6 \Omega$

Wkt: $X_C = \frac{1}{2\pi f C}$


$\therefore C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 5.6} = 5.68 \times 10^{-4} \text{ F}$

$C = 568 \mu\text{F}$

ii) work :- $P.f = \cos \phi = \frac{R}{Z} = \frac{19.19}{20} = 0.9595$ leading
 or $P.f = \cos \phi = \cos(-16.27) = 0.9595$ leading

iii) work :- $P = VI \cos \phi = 200 \times 10 \times 0.9595$
 $P = 1919.9 \text{ watt}$

Vector diagram :-

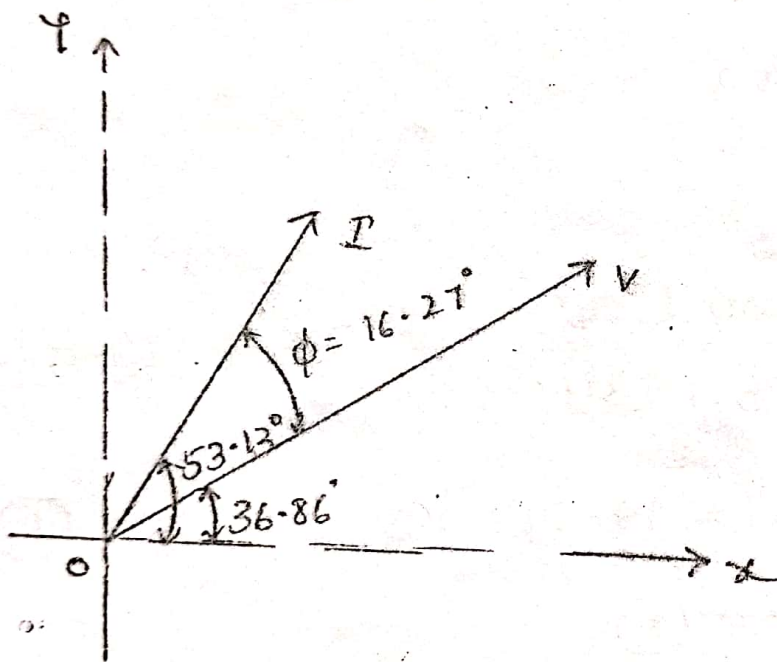

Ex (15) An voltage of $(40 - j30)V$ is applied to a circuit which carries a current of $(3 - j3)A$. Draw the vector diagram and find.

i) The elements of the circuit when the frequency is 50Hz
ii) power factor iii) power.

Solⁿ. Given :- $V = (40 - j30)V = 50 \angle -36.869^\circ V$

$$I = (3 - j3)A = 4.242 \angle -45^\circ A$$

i) Parameters of the circuit :-

Wkt :- $Z = \frac{V}{I} = \frac{50 \angle -36.869}{4.242 \angle -45} = 11.786 \angle -36.869 + 45$

$$Z = 11.786 \angle 8.131^\circ \Omega = (11.667 + j1.666) \Omega \quad \text{--- (1)}$$

Wkt :- $Z = R + jX_L$ --- (2)

Compare (1) & (2) we get

$$\boxed{R = 11.667 \Omega}$$

$$X_L = 1.666 \Omega$$

Wkt :- $X_L = 2\pi fL$

$$L = \frac{X_L}{2\pi f} = \frac{1.666}{2\pi \times 50} = 5.3 \times 10^{-3} H$$

$$\boxed{L = 5.3 \text{ mH}}$$

ii) Power Wkt :- $P.f = \cos \phi = \frac{R}{Z} = \frac{11.667}{11.786} = 0.9899$


$$\boxed{P.f = 0.9899 \text{ lagging}}$$

or $P.f = \cos(8.131) = 0.9899 \text{ lagging}$

iii) work :- $P = VI \cos \phi = 50 \times 4.242 \times 0.9899 = 209.9 \text{ W}$

$P = 210 \text{ Watts}$

iv) Vector diagram :-

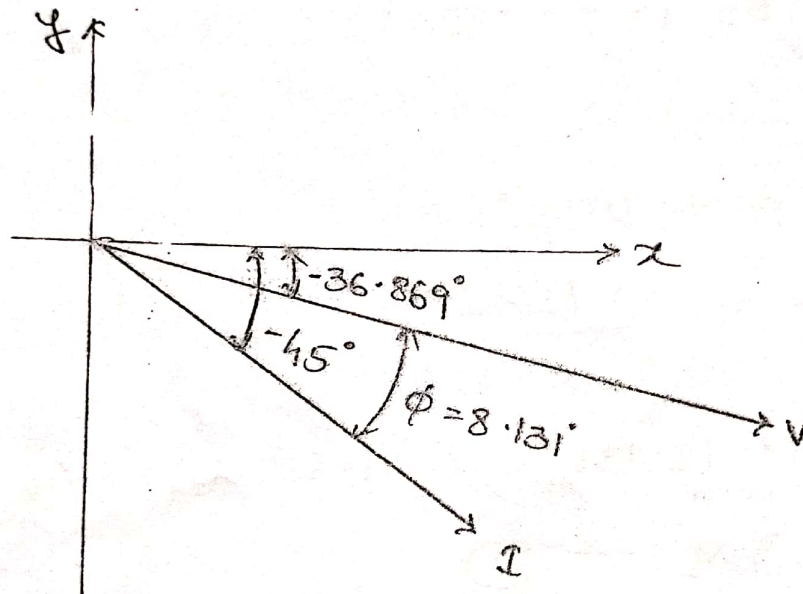


Question paper Numericals of 1 ϕ AC Circuits.

- Q 4) A voltage $V = 100 \sin 314t$ is applied to a circuit consisting of $25\text{-}\Omega$ resistor and $80\text{ }\mu\text{F}$ capacitor in series. Determine i) Peak value of current ii) power factor iii) Total power consumed by the circuit.

Solⁿ:

Given :-

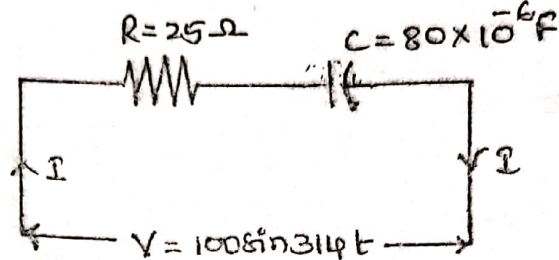

Dec/Jan 2015 (8 marks)

Find:-

- i) $I_m = ?$
 ii) $P.f = ?$
 iii) $P = ?$

Given that :- $V = 100 \sin 314t$ — (1)

Wkt :- $V = V_m \sin \omega t$ — (2)

Compare (1) & (2)

$\Rightarrow V_m = 100\text{ V}$

$\Rightarrow V_{rms} = V = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71\text{ V}$

$\Rightarrow \omega = 2\pi f = 314$

$f = \frac{314}{2\pi} = 50\text{ Hz}$

$\Rightarrow X_c = \frac{1}{2\pi f C} = \frac{10^6}{2\pi \times 50 \times 80}$

$X_c = 39.788\text{ }\Omega$

$\Rightarrow Z = \sqrt{R^2 + X_c^2} = \sqrt{(25)^2 + (39.788)^2} = 46.99\text{ }\Omega$

i) Wkt :- $I_m = \frac{V_m}{Z} = \frac{100}{46.99} = 2.128\text{ A}$

$I_m = 2.128\text{ A}$

Wkt :- $I = \frac{V}{Z} = \frac{70.71}{46.99} = 1.505\text{ A}$

or $I = I_m / \sqrt{2} = 2.12 / \sqrt{2} = 1.505\text{ A}$

ii) Wkt :- $P.f = \cos \phi = R/Z = 25/46.99 = 0.532$

$P.f = 0.532$ leading

iii) Wkt :- $P = VI \cos \phi = 70.71 \times 1.5 \times 0.532$

$P = 56.426\text{ Watts}$

Q2) Also find voltage across the capacitor when current is half of its maximum value (June/July 2018) (8 marks)

Solⁿ Wkt $I_m = \frac{V_m}{Z} = \frac{100}{46.99} = 2.128 \text{ A}$

$$I = \frac{1}{2} \times I_m \text{ (ie; half of Max^m current)}$$

$$I = \frac{2.128}{2} = 1.064 \text{ A}$$

Wkt:- $V_c = I \times X_c = 1.064 \times 39.788$


$$V_c = 42.33 \text{ V}$$

3

A voltage of 200V is applied to a series circuit consisting of a resistor, an inductor and capacitor. The respective voltages across these components are 170V, 150V & 100V and the current is 4A. Find: i) power factor ii) resistance iii) impedance iv) inductive reactance & capacitive reactance

Dec 24/2015 (8 marks)

Given:-

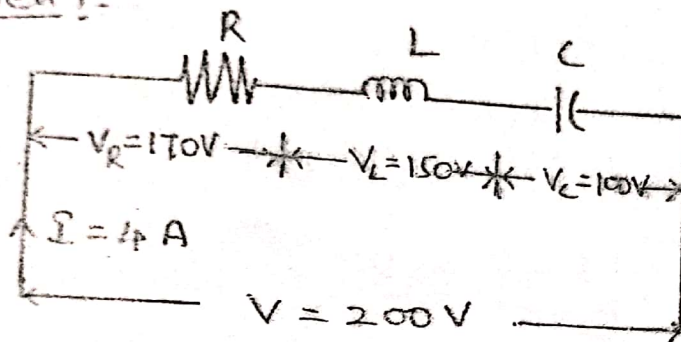

Find:-

- i) P.f ii) R iii) Z
iv) X_L v) X_C

iii) work:- $Z = \frac{V}{I} = \frac{200}{4} = 50 \Omega$

$Z = 50 \Omega$

ii) work:- $R = \frac{V_R}{I} = \frac{170}{4} = 42.5 \Omega$ ie; $R = 42.5 \Omega$

iv) work:- $X_L = \frac{V_L}{I} = \frac{150}{4} = 37.5 \Omega$ ie; $X_L = 37.5 \Omega$

v) work:- $X_C = \frac{V_C}{I} = \frac{100}{4} = 25 \Omega$ ie; $X_C = 25 \Omega$


i) work:- $P.f = \cos \phi = \frac{R}{Z} = \frac{42.5}{50} = 0.85$

$P.f = 0.85$ lagging

$\because X_L > X_C$

Q5 Find an expression for the current and calculate power when a voltage $V = 300 \sin 100\pi t$ is applied to a coil having $R = 60 \Omega$ and $L = 0.16 \text{ H}$.
June/July 2016 (8 marks)

Soln: Given:-

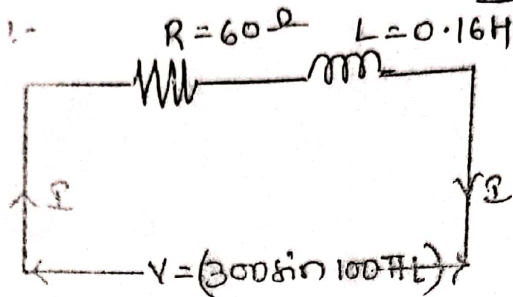

find:-

i) $I = ? \rightarrow$ expression

ii) $P = ?$

Given that $V = 300 \sin 100\pi t$ — (1)

or $V = V_m \sin \omega t$ — (2)

Compare (1) & (2)

$$\therefore V_m = 300 \text{ V}$$

$$\therefore V = \frac{V_m}{\sqrt{2}} = \frac{300}{\sqrt{2}} = 212.13 \text{ V}$$

$$\omega = 2\pi f = 100\pi$$

$$\therefore f = \frac{100\pi}{2\pi} = 50 \text{ Hz}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.16 = 50.265 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(60)^2 + (50.262)^2} = 78.27 \Omega$$

$$\text{or } \underline{\omega \text{kt}}: I = \frac{V}{Z} = \frac{212.13}{78.27} = 2.71 \text{ A}$$

$$I_m = 3.832 \text{ A} \Rightarrow (\because I_m = I \times \sqrt{2})$$

$$\underline{\omega \text{kt}} \text{ p.f.} = \cos \phi = \frac{R}{Z} = \frac{60}{78.27} = 0.766 \text{ lagging}$$

$$\therefore \phi = \cos^{-1}(0.766) = 40^\circ$$

or:

$$I = I_m \sin(\omega t - \phi)$$

$$I = 3.832 \sin(100\pi t - 40^\circ) \text{ A}$$

$$\text{ii) } \underline{\omega \text{kt}}: P = VI \cos \phi = 212.13 \times 2.71 \times 0.766$$

$$P = 440.39 \text{ W}$$

Ex ⑥ An alternating voltage $(80 + j60) \text{ V}$ is applied to a circuit and the current flowing is $(-4 + j10) \text{ A}$. find:
 i) the impedance of the circuit ii) the phase angle
 iii) power consumed. Dec 2015/2016 (5 marks)

Solⁿ

Given 1. $V = (80 + j60) \text{ V} = 100 \angle 36.86^\circ \text{ V}$

$I = (-4 + j10) \text{ A} = 10.77 \angle 111.80^\circ \text{ A}$

find :- i) $Z = ?$ ii) $\phi = ?$ iii) $P = ?$

i) Wkt $Z = \frac{V}{I} = \frac{100 \angle 36.86^\circ}{10.77 \angle 111.80^\circ} = 0.928 \angle -74.94^\circ$

$Z = 0.928 \angle -74.94^\circ \Omega$

ii) Wkt $\therefore \phi = \phi_1 - \phi_2 = 36.86 - 111.8 = -74.94^\circ$

$\phi = 74.94^\circ$ (-ve sign represents ϕ lags V/I)

iii) Wkt $P = V I \cos \phi = 100 \angle 36.86^\circ \times 10.77 \angle 111.8^\circ \times \cos(-74.94^\circ)$


~~$P = 1077$~~

$P = 100 \times 10.77 \times \cos(-74.94^\circ)$

$P = 279.83 \text{ watts}$

Ex (9) A resonant series circuit with $R = 5\Omega$, $L = 1\text{mH}$ and $C = 0.001\mu\text{F}$ is connected to a 100V supply. find.
 i) the drop across L and ii) drop across C .
 Take the supply as reference phasor.

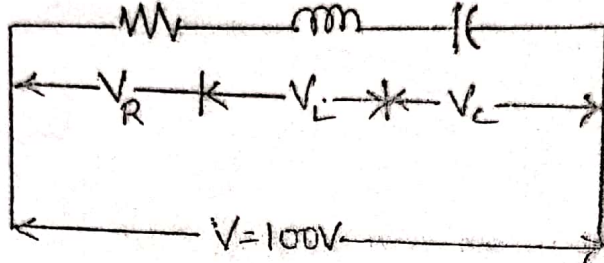Soln: Given:- $R = 5\Omega$ $L = 1\text{mH}$ $C = 0.001\mu\text{F}$



find:-

i) $V_L = ?$

ii) $V_C = ?$

Assume $f = 50\text{Hz}$

Given that $L = 1 \times 10^{-3}\text{H}$

$C = 0.001 \times 10^{-6}\text{F}$

$\therefore X_L = 2\pi fL = 2\pi \times 50 \times 10^{-3}$

$X_L = 314.15 \times 10^{-3} \Omega \approx 0.31415\Omega$

$X_C = \frac{1}{2\pi fC} = \frac{10^6}{2\pi \times 50 \times 0.001} = 3183098.862\Omega$

$X_C > X_L$

$\therefore Z = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{(5)^2 + (3183098.862 - 0.314)^2}$

$Z = 3183098.548\Omega$

$\therefore I = \frac{V}{Z} = \frac{100}{3183098.548} = 3.141 \times 10^{-5}\text{A}$

i) wkt $V_L = I X_L = 3.141 \times 10^{-5} \times 0.3141$

$V_L = 9.867 \times 10^{-6}\text{V}$

ii) wkt $V_C = I X_C = 3.141 \times 10^{-5} \times 3183098.862$


$V_C = 99.98\text{V}$

Module 2 THREE PHASE BALANCED CIRCUITS

I Introduction :- Advantages of 3 ϕ circuits.

- *> The output of 3 ϕ Machine is always greater than 1 ϕ Machine i.e. 1.5 times for same size of Machine.
- *> 3 ϕ Machine occupies less space and less cost.
- *> For transmission and distribution 3 ϕ system needs less copper hence economical
- *> It is possible to produce RM by using 3 ϕ system.
- *> 3 ϕ system gives steady output and improved power factor

Generation of 3 ϕ voltage :-

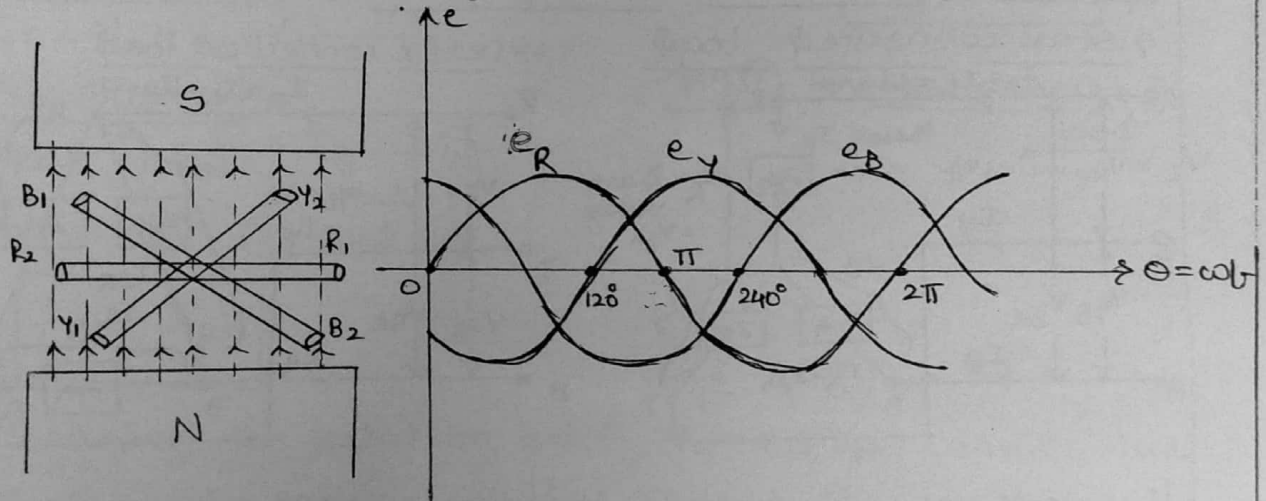

- *> The three coils (windings) are placed in a magnetic field named as R (Red), Y (Yellow), B (Blue).
- *> Let e_R , e_Y , e_B are the three voltages induced in the coils R, Y, B.
- *> All the three coils are displaced by 120° electrical.
- *> Suppose if e_R is assumed to be the reference and is zero for the instant shown in waveform then at the same time e_Y will be displaced by 120° from e_R & e_B will be displaced by 240° from e_R or 120° from e_B .


The mathematical eqⁿs are

$$e_R = E_m \sin \omega t$$

$$e_Y = E_m \sin (\omega t - 120^\circ)$$

$$e_B = E_m \sin (\omega t - 240^\circ)$$
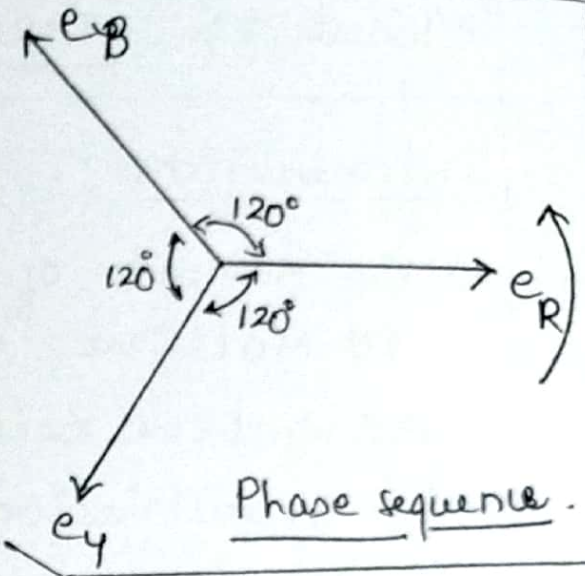
$$\therefore \bar{e}_R + \bar{e}_Y + \bar{e}_B = 0$$



Q17 Define phase sequence of 3 ϕ AC (2m)

Defⁿ

The sequence in which the voltages reach their maximum +ve value is called phase sequence.

Star connected load

Line values

* Line current (I_L)

$$I_R = I_Y = I_B = I_L$$

* Line voltage (V_L)

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

Phase values

* Phase current (I_{ph})

$$I_R = I_Y = I_B = I_{ph}$$

* Phase voltage (V_{ph})

$$V_R = V_Y = V_B = V_{ph}$$

In star connected load .

* Line current = Phase current .


ie; $I_L = I_{ph}$ Amps

* Line voltage = $\sqrt{3}$ times of Phase voltage .


ie; $V_L = \sqrt{3} V_{ph}$ volts

* The Power $P = \sqrt{3} V_L I_L \cos \phi$ Watts .

Where $\cos \phi$ - Power factor .

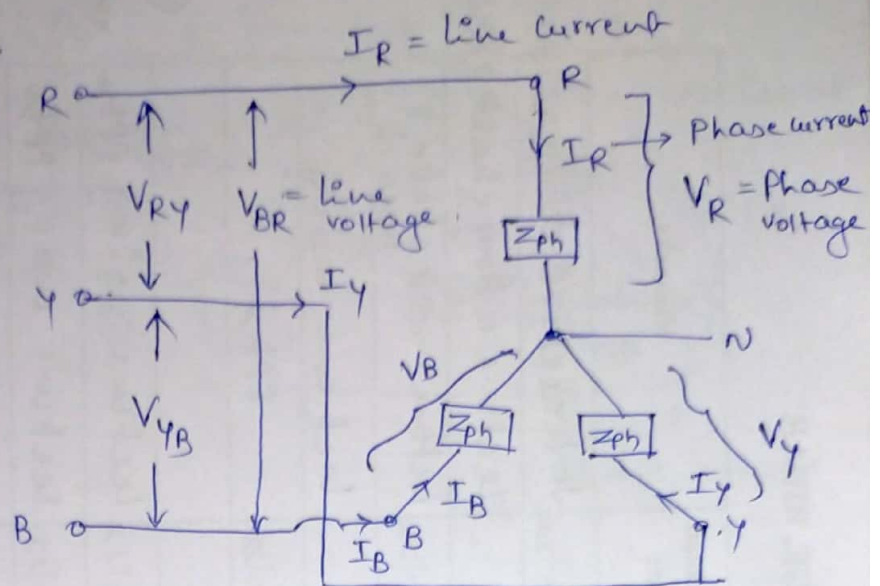

Delta connected load

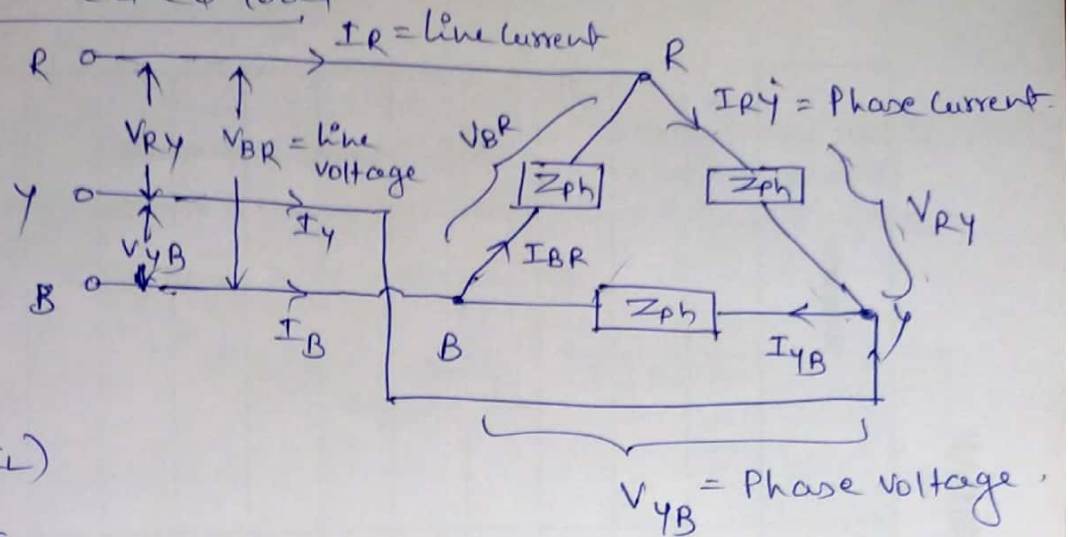

Line values

*> Line current (I_L)

$$I_R = I_Y = I_B = I_L$$

*> Line voltage (V_L)

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

Phase values

*> Phase current (I_{ph})

$$I_{RY} = I_{YB} = I_{BR} = I_{ph}$$

*> Phase voltage (V_{ph})

$$V_{RY} = V_{YB} = V_{BR} = V_{ph}$$

In Delta connected load .

*> Line voltage = Phase Voltage .

ie;
$$V_L = V_{ph} \quad \text{volts}$$

*> Line current = $\sqrt{3}$ times Phase current .

ie;
$$I_L = \sqrt{3} I_{ph} \quad \text{Amps}$$

*> The power
$$P = \sqrt{3} V_L I_L \cos \phi \quad \text{watts .}$$

where $\cos \phi$ - Power factor .